


VLSI studens Internal talks

TDC and Hysteresis Comparator

Alberto Riccardi
 
# Clock resolution



$$2^9 = 512 \quad \longrightarrow \quad 6.25\text{ns} \quad \bullet \quad 512 = 3.2\mu\text{s}$$



Since the rate per strip is about 30 kHz the biggest signal is exhausted in 3.2 $\mu\text{s}$ , so we have a pile-up problem.


We want a system that has 1LSB = 400ps

# Goals

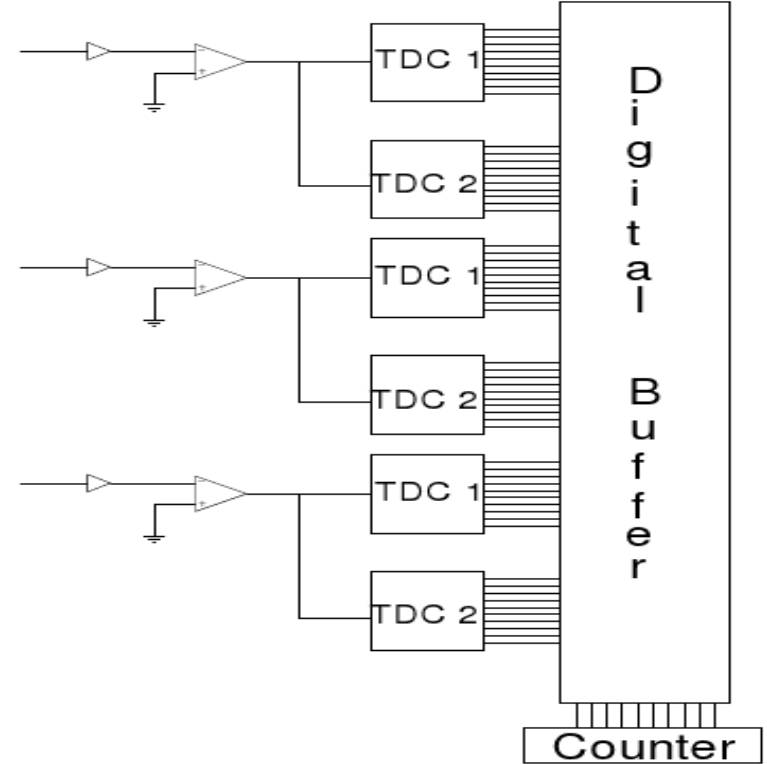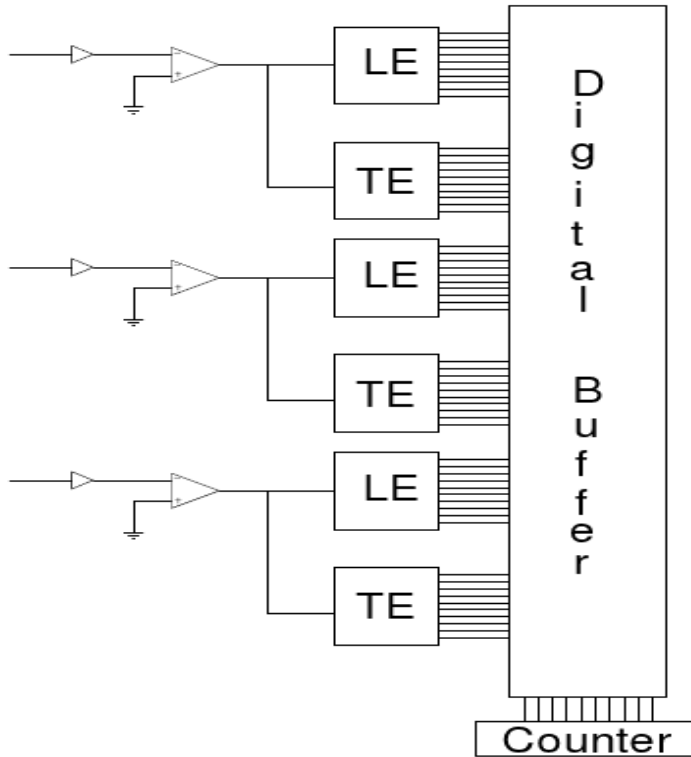


- Redesign and optimization the TDC
- Investigation about new technology

# Time to Digital Converter


 


- Accurate
- Low power
- Compact
- Slow



# Wilkinson ADC

 



# TDC implementation

  

# TDC implementation

  


# TDC implementation

  




# Timing

 


With this system we obtain that  $1\text{LSB} = 49\text{ps}$ , since we have  $6.25\text{ns}/128$

# Double cascode current mirror

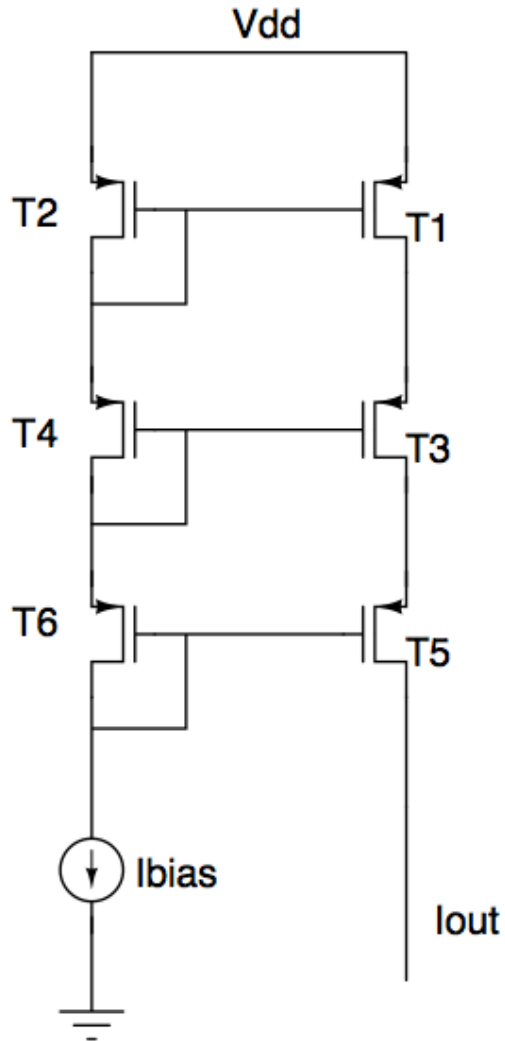


$$r_{out} \approx g_{m5} r_{o5} r_{out1} = g_{m5} r_{o5} g_{m3} r_{o3} r_{o1} \approx 550 M\Omega$$


# Transistor level implementation

 


# Current sweep

 


# Time to Amplitude Converter

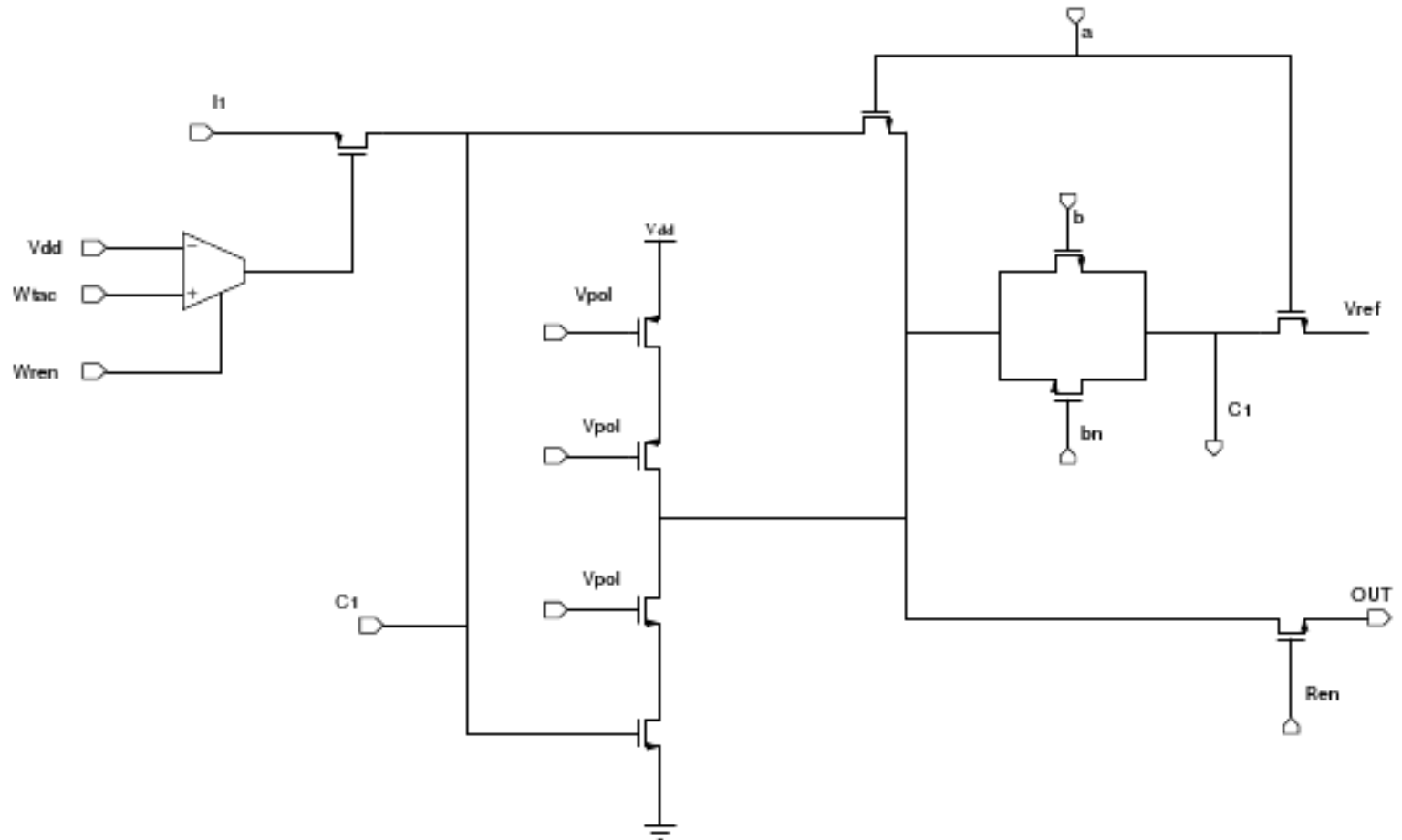

# Time to Amplitude Converter

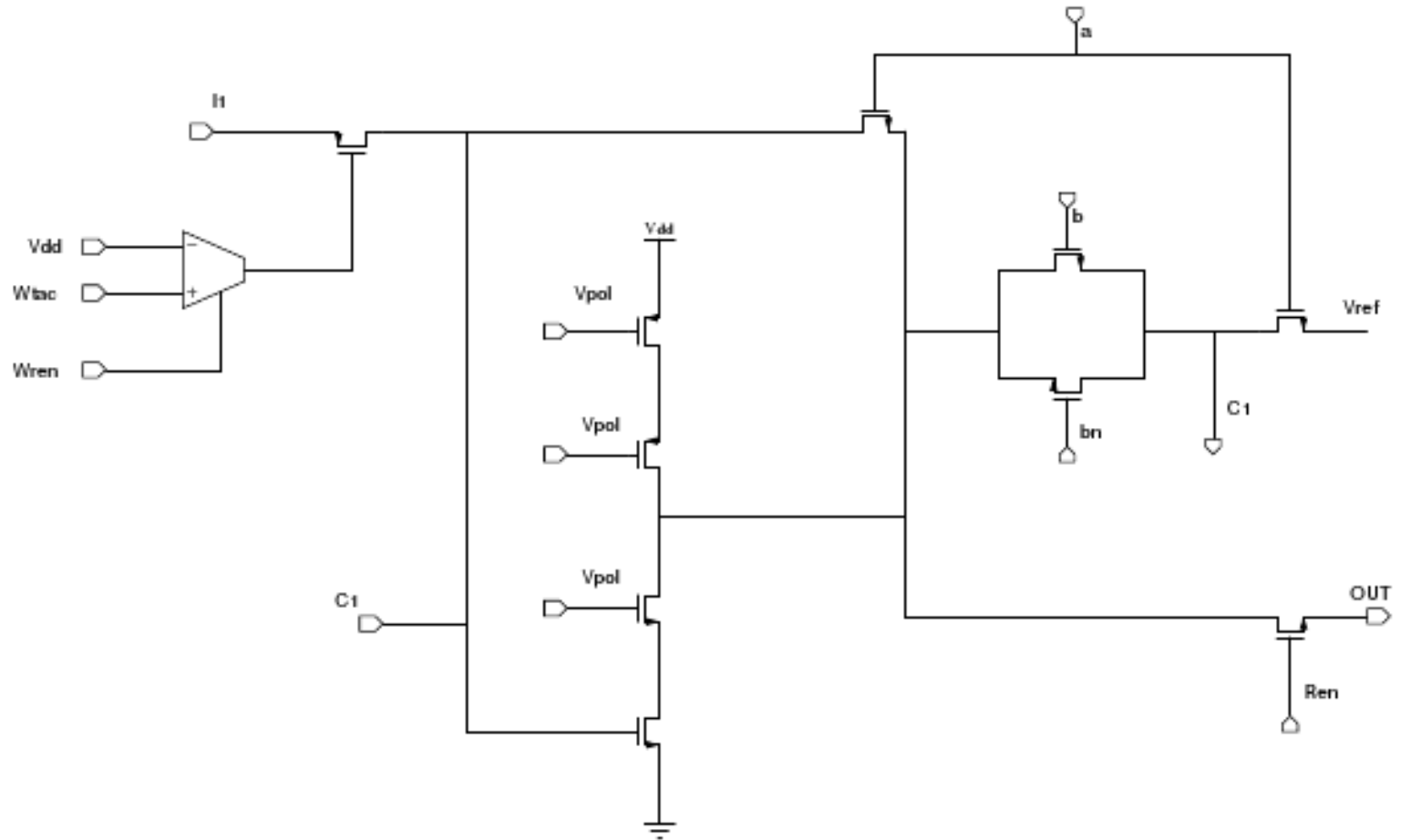


# Hysteresis Comparator II

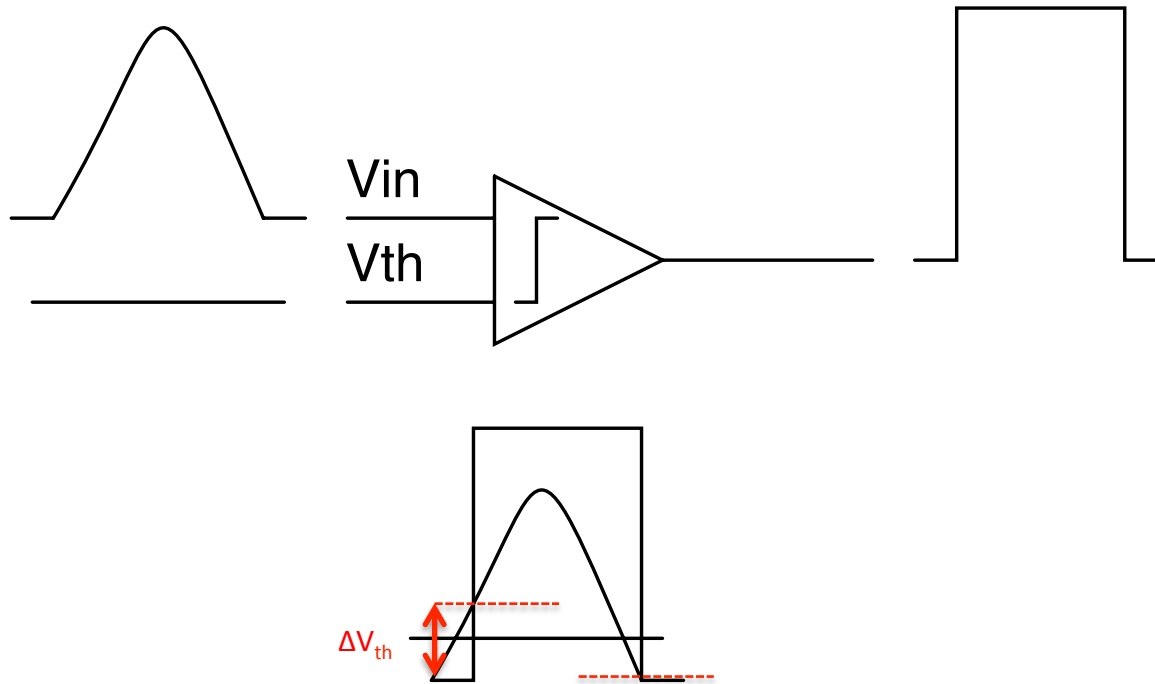

The output doesn't fire when the signal reaches the set threshold.

# Hysteresis Comparator Transistor Level

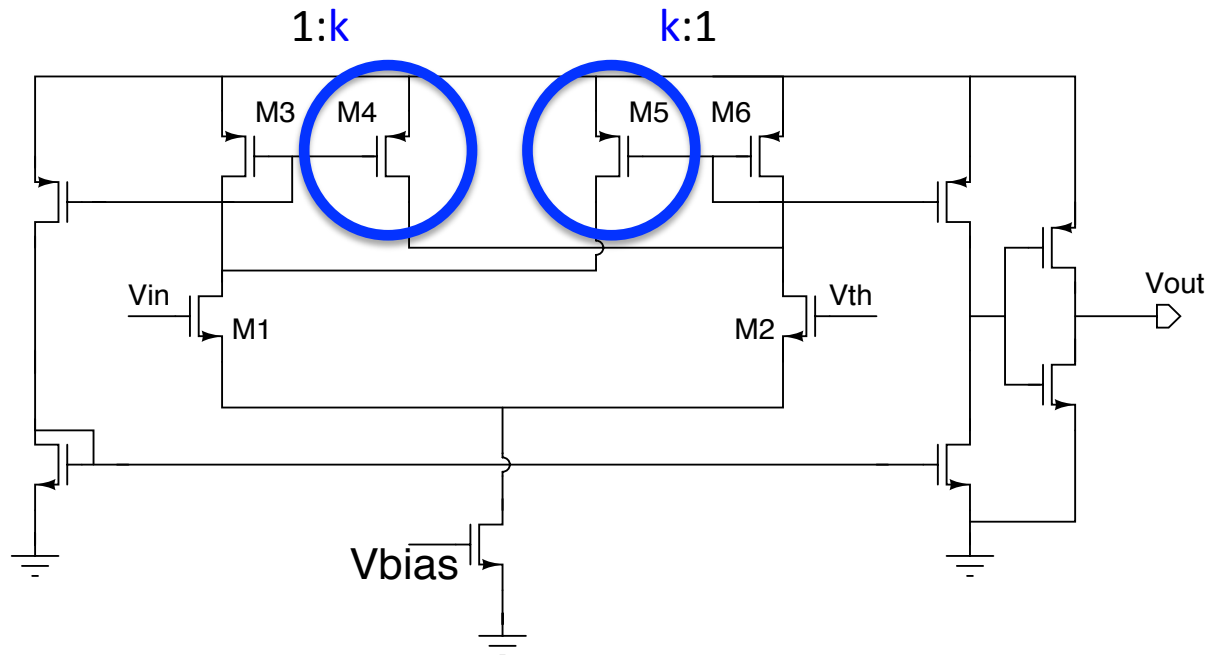

In the “classic” comparator the output changes when the current flowing into M1 is equal to the one into M2

In the hysteresis comparator we don't have this effect




# Hysteresis Comparator Current

➤  $i_{M1} = i_{M5}$

➤  $i_{M2} = i_{M4}$

➤  $i_{M5} = k * i_{M6} = k * i_{M2}$


➤  $i_{M1} + i_{M2} = i_{bias}$

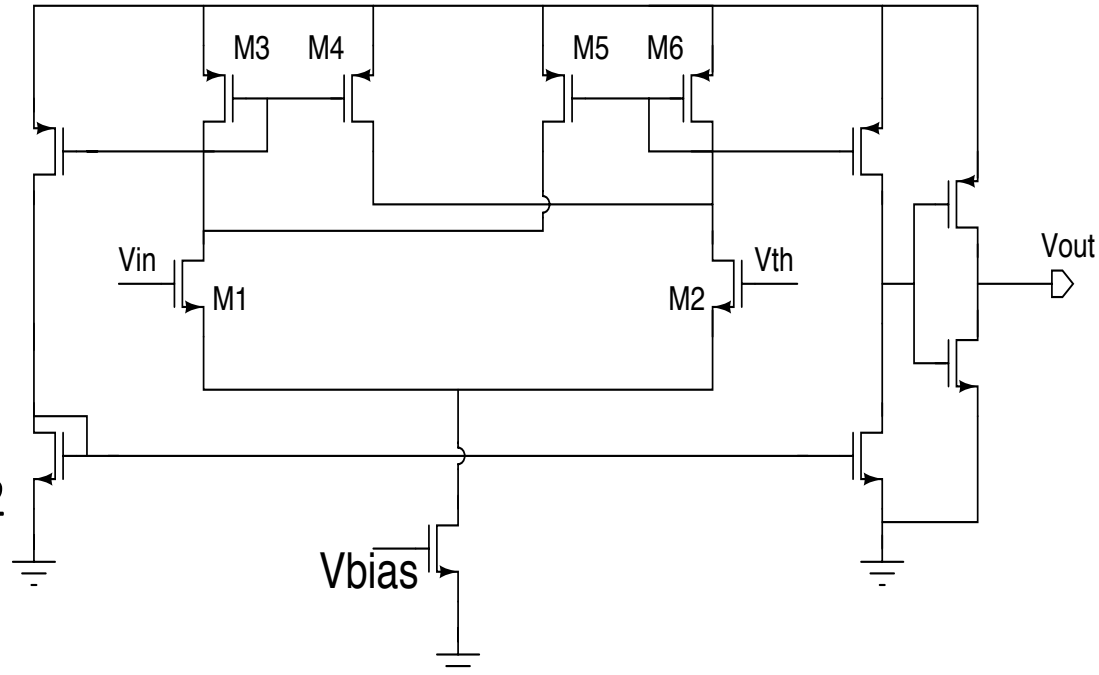

- $i_{M1} = k/(1+k) i_{bias}$

- $i_{M2} = 1/(1+k) i_{bias}$


# Single to Differential Stage

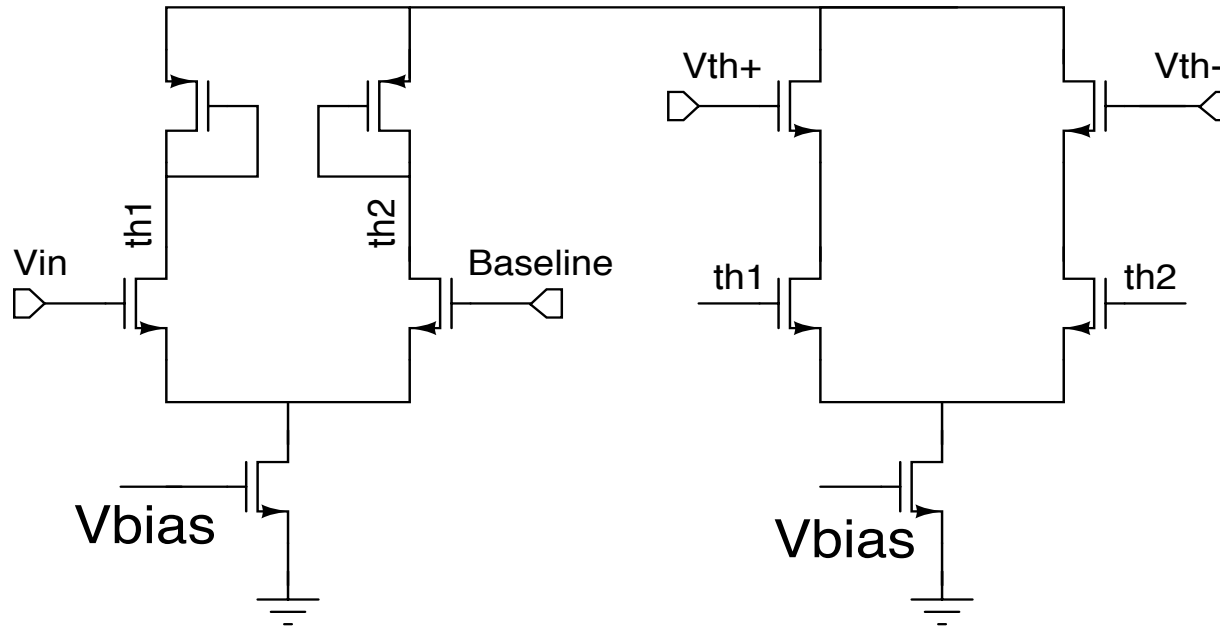


- The first part converts  $V_{in}$  from single ended to differential
- The second part is necessary to set a differential threshold

# Complete Hysteresis Comparator

Differential Stage

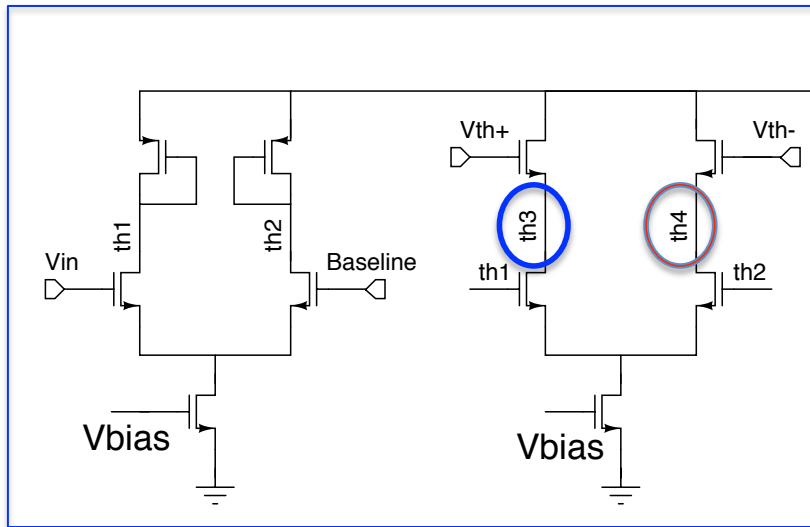

Comparator Stage

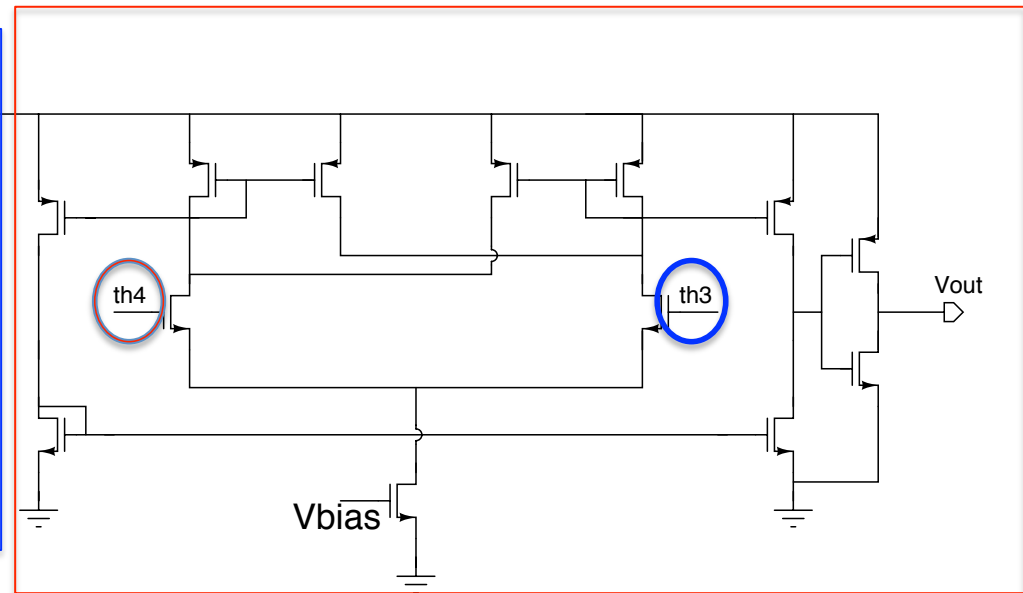


# Theoretical Threshold


$A = 2.612$

Baseline = 700 mV


$(V_{th+} - V_{th-}) = 60 \text{ mV}$

 

 
$$V_{th} = 22.89 \text{ mV} + \text{Baseline}$$



# Hysteresis Comparator II

 


Without Hysteresis

 

With Hysteresis
 
# Sweep Threshold


$V_{th+} - V_{th-}$
10mV
20mV
30mV
40mV
50mV



# Differential DAC

Standard configuration: 10

B1 B0

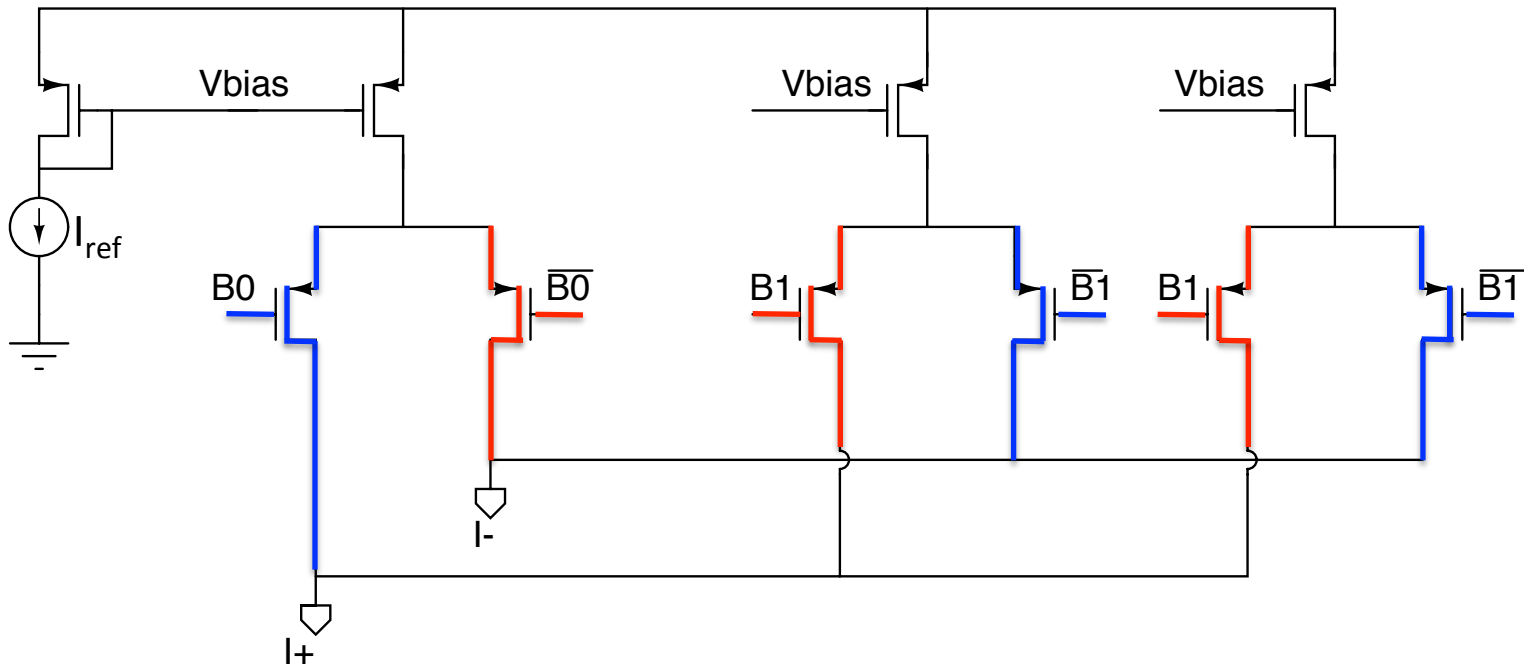


$$I_- = 2 I_{ref}$$

$$I_+ = 1 I_{ref}$$

# Differential DAC

Standard configuration: **11**

B1 B0

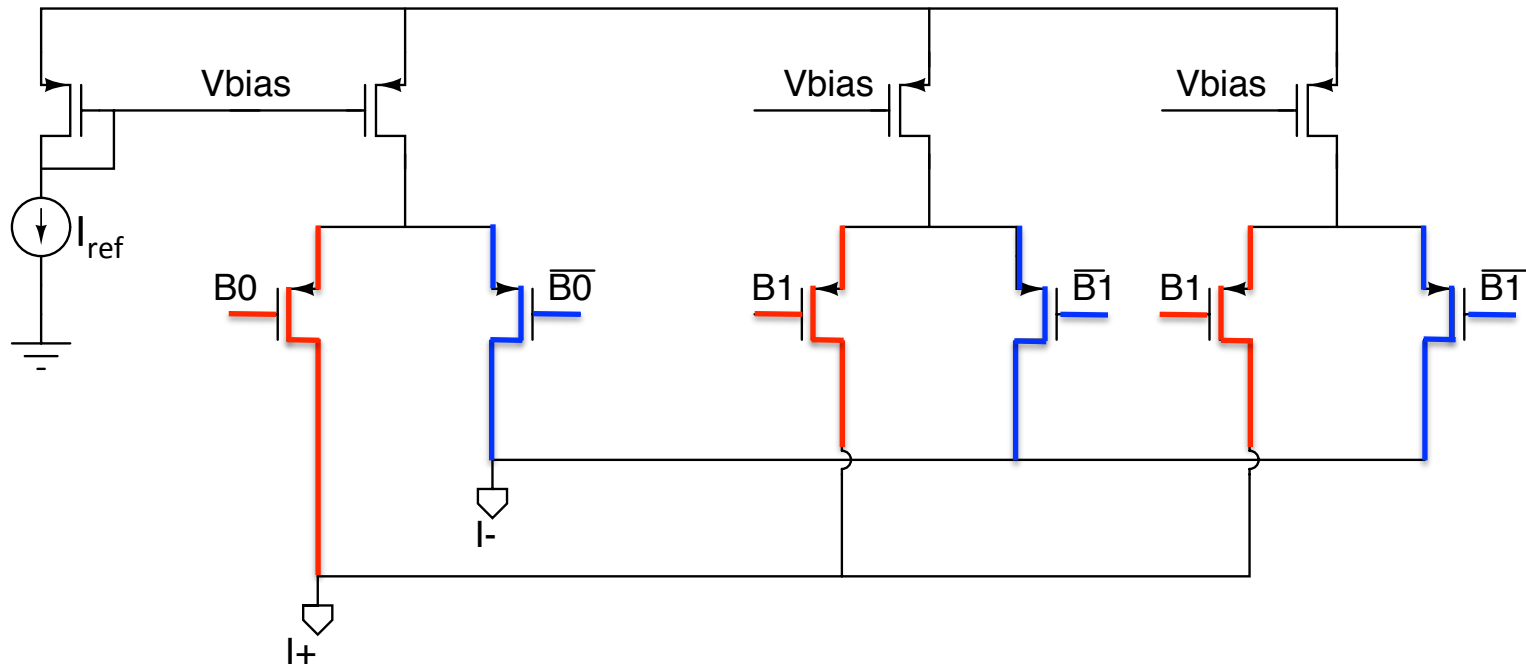


$$I_- = 3 I_{ref}$$

$$I_+ = 0 I_{ref}$$




# Nonlinearity

 


LSB → DNL [mV]

-LSB →

 

LSB → INL [mV]

INL

 

DNL = differential nonlinearity

INL = integral nonlinearity