



# Front-end design in CMOS for high resolution detectors

**Gianluigi De Geronimo**

[degeronimo@bnl.gov](mailto:degeronimo@bnl.gov)

*Brookhaven National Laboratory, Upton, NY 11973, USA*

*November 2013*

# Outline



- I. Input MOSFET optimization
- II. Amplifier design
- III. Charge amplification
- IV. Filter design

**Part I**

# **Input MOSFET optimization**
 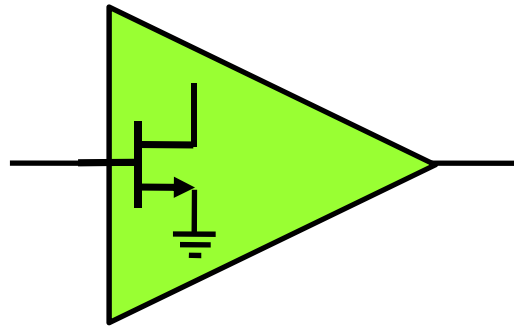
# Dominant noise sources

In a properly designed **amplifier**, the dominant noise sources are from the **input transistor**. The other noise sources (e.g. from the cascode, load, etc.) are made negligible.




The parameters relevant to the resolution are the **equivalent input noise sources** (series and parallel) and the **input capacitance**.

Basic MOSFET model:


$$S_{vA} \approx \frac{S_{vf1}}{f} + \gamma n \frac{4kT}{g_m} \quad \left\{ \begin{array}{l} n = \frac{g_{mS}}{g_m} \approx 1.25 \approx \text{subth.slope} \\ \gamma = 1/2 - 2/3 \text{ (WI - SI)} \end{array} \right.$$

$$S_{iA} \approx \text{negligible}$$

$$C_G \approx C_{GS} + C_{GD}$$

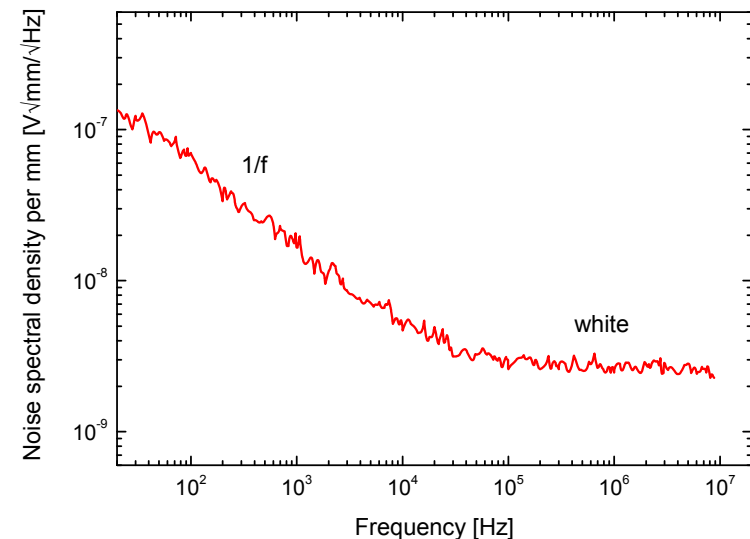

## Equivalent Noise Charge (ENC)

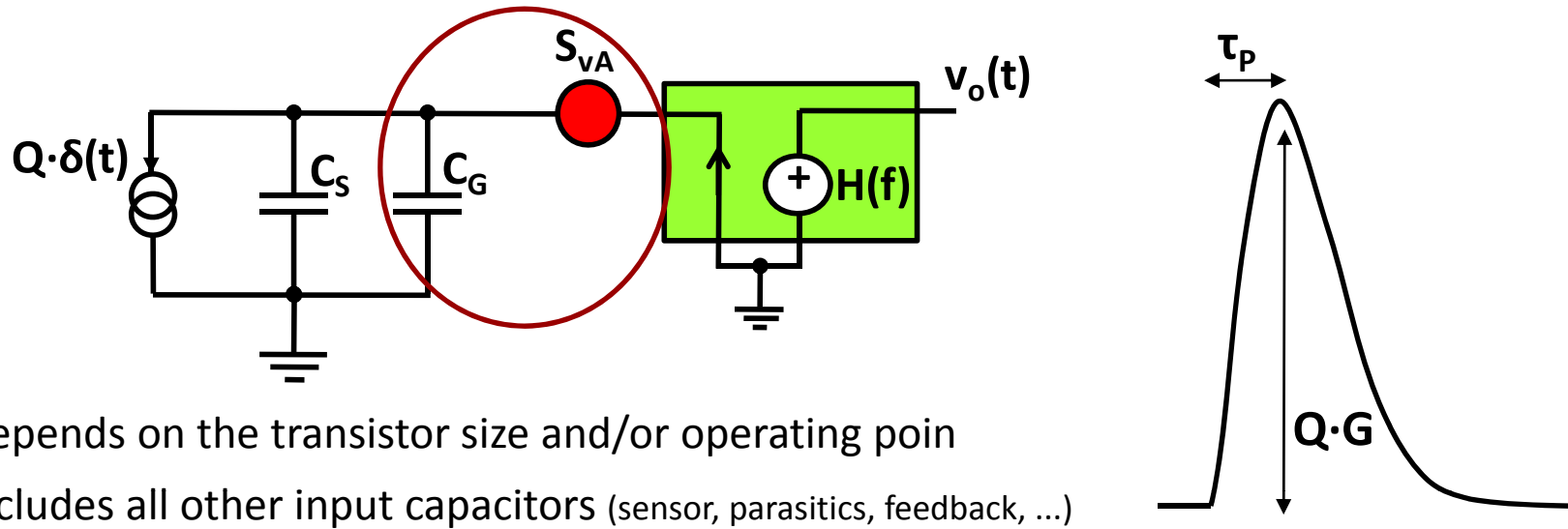

$$\text{Equivalent Noise Charge (ENC)} = V_{\text{orms}}/G$$

$$\text{ENC}^2 = 2\pi A_{\text{vfp}} S_{\text{vf1}} (C_S + C_G)^2 + \frac{A_{\text{vwP}}}{\tau_P} \gamma n \frac{4kT}{g_m} (C_S + C_G)^2$$

Typical values  $A_{\text{vfp}} \approx 0.5$ ,  $A_{\text{vwP}} \approx 1$  (for unilateral power spectral densities)

G. De Geronimo et al., IEEE TNS 52 (2005)

**We must optimize the input MOSFET ( $L, W, i_{\text{dw}}$ )**

# MOSFET model: densities

We model  $C_G$  and  $S_{VA}$  as **functions of gate size (L, W)** and drain current density  $i_{DW}$

$$C_G \approx C_{GS} + C_{GD} + C_{GB} \approx c_{GWL} WL \approx c_{ox} WL$$

$c_{GWL}$  = gate capacitance per unit area  
 $c_{ox}$  = gate oxide capacitance per unit area

$$S_{VA} \approx \frac{S_{vf1}}{f} + \gamma n \frac{4kT}{g_m} = \frac{K_f}{c_{ox} WL \cdot f} + \gamma n \frac{4kT}{g_{mW}(i_{DW}, L)W}$$

$K_f$  = 1/f coeff. per unit area (weakly dep. on  $i_{DW}$ , L)  
 $\gamma$  = gamma coefficient (function of  $i_{DW}$ )  
 $g_{mW} = g_m$  per unit W (function of  $i_{DW}$ , L)  
 $i_{DW} = I_D$  per unit W (drain current density)

If we use the following **basic MOSFET equations**

$$I_D \approx \begin{cases} \frac{1}{2n} \mu c_{ox} \frac{W}{L} (V_{GS} - V_{th})^2 & \text{SI (strong inv.)} \\ \mu c_{ox} V_T^2 \frac{W}{L} \exp\left(\frac{V_{GS} - V_{th}}{nV_T}\right) & \text{WI (weak inv.)} \end{cases}$$

we can express the  $g_m$  as

$$g_m = g_{mW} W \approx \begin{cases} \sqrt{\frac{2\mu c_{ox}}{n} \frac{W}{L} I_D} = W \sqrt{\frac{2\mu c_{ox}}{n} \frac{i_{DW}}{L}} & \text{SI} \\ \frac{\mu c_{ox} V_T}{n} \frac{W}{L} \exp\left(\frac{V_{GS} - V_{th}}{nV_T}\right) = \frac{I_D}{nV_T} = W \frac{i_{DW}}{nV_T} & \text{WI} \end{cases}$$

## Low-frequency noise vs L,W



To a first order, we can assume that the change  $\Delta I$  in current due to **trapping / de-trapping** is **inversely proportional to the transit time** (speed of the device).

$$\Delta I \div \frac{1}{\tau} = \omega_T = 2\pi f_T$$

The superposition of the uncorrelated trapping / de-trapping events is, in power, **proportional to the area of the gate**, i.e. WL.

$$\Delta I^2 \div \omega_T^2 WL$$

Hence, the power spectrum (associated to the drain current) at the output of the FET has the same dependence.

$$S_{i_o} \div \omega_T^2 WL$$

We can **bring it to the input**, dividing by  $g_m^2$  (note:  $g_m \approx \omega_T C_G$ ):

$$S_{v_i} = \frac{S_{i_o}}{g_m^2} \div \frac{\omega_T^2 WL}{\omega_T^2 W^2 L^2} = \frac{1}{WL} \quad \longrightarrow \quad \frac{S_{v_f1}}{f} = \frac{S_{v_f1WL}(i_{DW}, L)}{WL \cdot f} \approx \frac{S_{v_f1WL}}{WL \cdot f}$$

*(i) Due to short channel effects, deep submicron MOSFETs may show a dependence of  $S_{v_f1WL}$  on L and  $i_{DW}$ . (ii) Alternative theories consider the mobility fluctuation.*

# Optimization in absence of power constraint

The contribution of the MOSFET to the ENC can be written as follows:

$$ENC^2 = 2\pi A_{vfp} \frac{K_f}{c_{ox} L_{min}} \frac{(C_S + c_{ox} W L_{min})^2}{W} + \begin{cases} \frac{A_{vwp}}{\tau_P} 4kT \gamma n^{3/2} \sqrt{\frac{L_{min}}{2\mu c_{ox}}} \frac{1}{\sqrt{i_{DW}}} \frac{(C_S + c_{ox} W L_{min})^2}{W} & \text{SI} \\ \frac{A_{vwp}}{\tau_P} 4kT \gamma n^2 V_T \frac{1}{i_{DW}} \frac{(C_S + c_{ox} W L_{min})^2}{W} & \text{WI} \end{cases}$$

- We operate the MOSFET in SI and select  $i_{DW} = i_{DWmax}$  ( $i_{DW}$  at maximum  $V_{GS} - V_{th}$ )
- The series term is minimized for  $L = L_{min}$
- The white and 1/f terms are minimized for  $W = C_S / c_{ox} L$  or  $C_G = C_S$  (**capacitive matching**)

The  $ENC_{min}$  (i.e. the ENC at maximum power and optimum W) can be written as:

$$ENC_{min}^2 = 4C_S \left( \frac{A_{vwp}}{\tau_P} 4kT \gamma n^{3/2} L_{min}^{3/2} \sqrt{\frac{c_{ox}}{2\mu}} \frac{1}{\sqrt{i_{DWmax}}} + 2\pi A_{vfp} K_f \right)$$

**Power prohibitively high** for almost all of practical cases



## With power constraint: moderate inversion

We impose a limit to the power dissipation  $I_D = i_{D0} W \leq I_{D0}$ . The ENC can be written as:

$$ENC^2 = 2\pi A_{vFP} \frac{K_f}{c_{ox} L_{min}} \frac{(C_S + c_{ox} W L_{min})^2}{W} + \begin{cases} \frac{A_{vFP}}{\tau_P} 4kT \gamma n^{3/2} \sqrt{\frac{L_{min}}{2\mu c_{ox}}} \frac{1}{\sqrt{I_{D0}}} \frac{(C_S + c_{ox} W L_{min})^2}{\sqrt{W}} & \text{SI} \\ \frac{A_{vFP}}{\tau_P} 4kT \gamma n^2 V_T \frac{1}{I_{D0}} (C_S + c_{ox} W L_{min})^2 & \text{WI} \end{cases}$$

- The 1/f term still has a minimum for  $W = C_S / c_{ox} L_{min}$  or  $C_G = C_S$  (capacitive matching)
- The white term has a minimum for:
  - $W = C_S / 3c_{ox} L_{min}$  or  $C_G = C_S / 3$  in strong inversion (SI)
  - $W \rightarrow 0$  or  $C_G = 0$  in weak inversion (WI) **note:  $W \rightarrow 0$  pushes back towards SI**

Most of the applications typically impose a limit of less (or much less) than 1 mW per pixel. With these constraints the input MOSFET frequently operates in **moderate inversion** (between weak and strong inversion).

The optimization requires a **model in the region of moderate inversion**.

# MOSFET in moderate inversion: $g_m$

## Transconductance $g_{mW}$

$$IC = \frac{i_{DW} L}{2nV_T^2 \mu c_{ox}} \quad \text{inversion coefficient}$$

$$g_{mW} \approx \begin{cases} \sqrt{\frac{2\mu c_{ox}}{n}} \frac{i_{DW}}{L} & IC > 10 \quad \text{SI} \\ \frac{i_{DW}}{nV_T} & IC < 0.1 \quad \text{WI} \\ ?? & 0.1 < IC < 10 \quad \text{MI} \end{cases}$$





(EKV)

$$g_{mW}(IC) \approx \frac{i_{DW}}{nV_T} \frac{\sqrt{1+4 \cdot IC} - 1}{2 \cdot IC} =$$

$$= \frac{V_T \mu c_{ox}}{L} (\sqrt{1+4 \cdot IC} - 1)$$

alternatively: extract from simulator

  

# MOSFET in moderate inversion: $\gamma$



## Gamma coefficient $\gamma$



$$IC = \frac{i_{DW}L}{2nV_T^2\mu c_{ox}} \quad \text{inversion coefficient}$$

$$\gamma \approx \begin{cases} \frac{2}{3} & IC > 10 \quad \text{SI} \\ \frac{1}{2} & IC < 0.1 \quad \text{WI} \\ ?? & 0.1 < IC < 10 \quad \text{MI} \end{cases}$$



(EKV)
  
$$\gamma(IC) \approx \frac{1}{1+IC} \left( \frac{1}{2} + \frac{2}{3}IC \right)$$



# MOSFET in moderate inversion: $C_G$

## Gate capacitance $C_G$


$$C_G \approx c_{ox} WL$$



$$C_G \approx 2c_{ov} W + \frac{2}{3} c_{ox} WL$$

$c_{ov}$  = drain/source overlap capacitance per unit W

 $c_{ov} \approx 0.5 \text{ fF}/\mu\text{m}$  for CMOS  $0.25\mu\text{m}$




(EKV)

$$\gamma_C(IC) \approx \left( \frac{3}{2} + \frac{1}{3} \frac{\sqrt{1 + 4 \cdot IC} + 1}{IC^2} \right)^{-2/3}$$

$$C_{GSW} \approx c_{ox} L \gamma_C(IC)$$

$$C_{GBW} \approx c_{ox} L \frac{n-1}{n} [1 - \gamma_C(IC)]$$

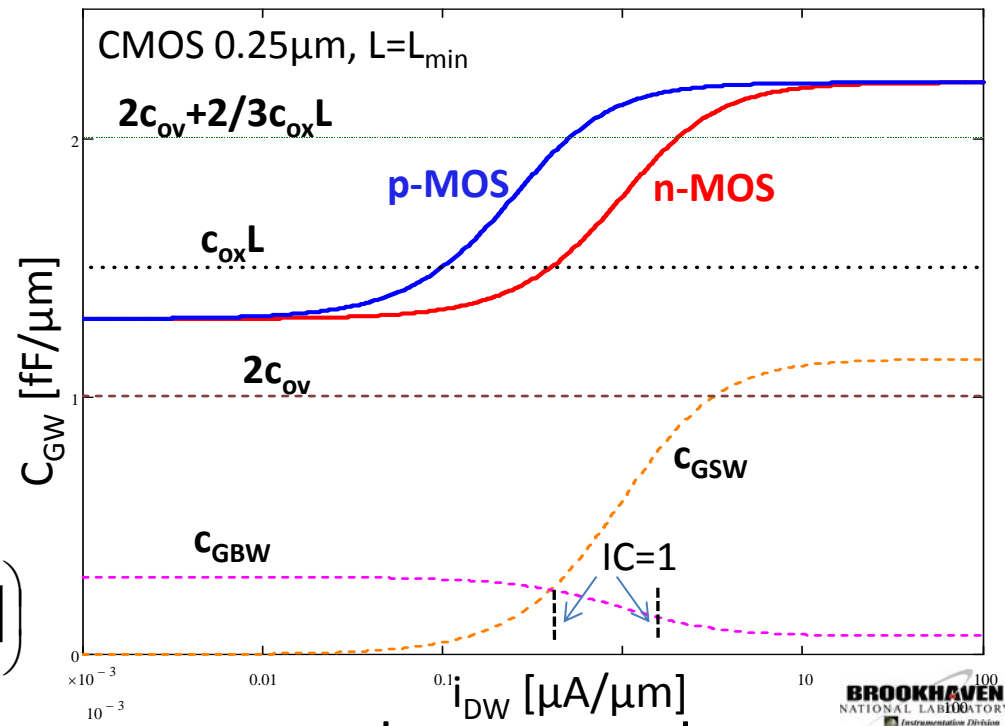
$$C_{GW} \approx 2c_{ov} + c_{ox} L \left( \gamma_C(IC) + \frac{n-1}{n} [1 - \gamma_C(IC)] \right)$$




# Low-frequency noise: amplitude and slope

The selected technology should be characterized for low-frequency noise

CMOS 250nm

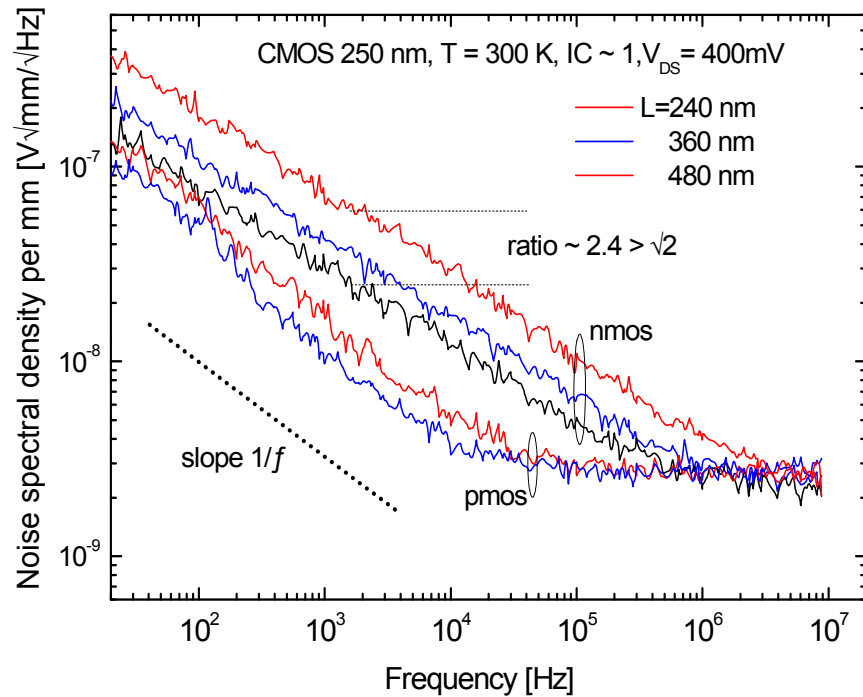

CMOS 180nm

 

Note slope of pmos vs nmos

$$S_{vA\_lf} \approx \frac{K_f}{C_{ox} WL \cdot f}$$

$$S_{vA\_lf} \approx \frac{K_f(IC,L)}{C_{ox} WL \cdot f^{\alpha_f(IC,L)}}$$




$$ENC_{lf}^2 = 2\pi A_{vfP} \frac{K_f(IC,L)}{C_{ox} WL} (C_S + C_G)^2$$

$$ENC_{lf}^2 = (2\pi)^\alpha \frac{A_{vfP}(\alpha)}{\tau^{1-\alpha_f(IC,L)}} \frac{K_f(IC,L)}{C_{ox} WL} (C_S + C_G)^2$$


# Low-frequency noise vs $i_{DW}$




## CMOS 250nm

 



## CMOS 180nm

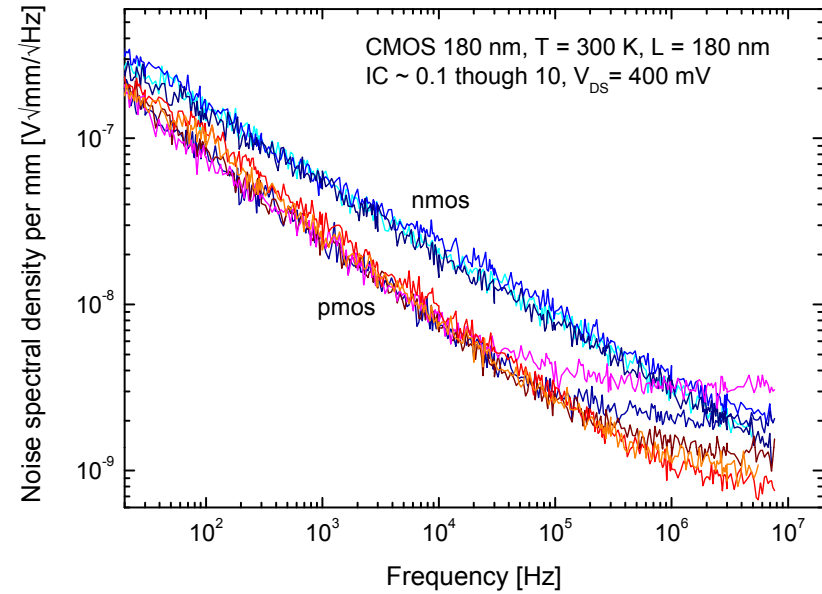

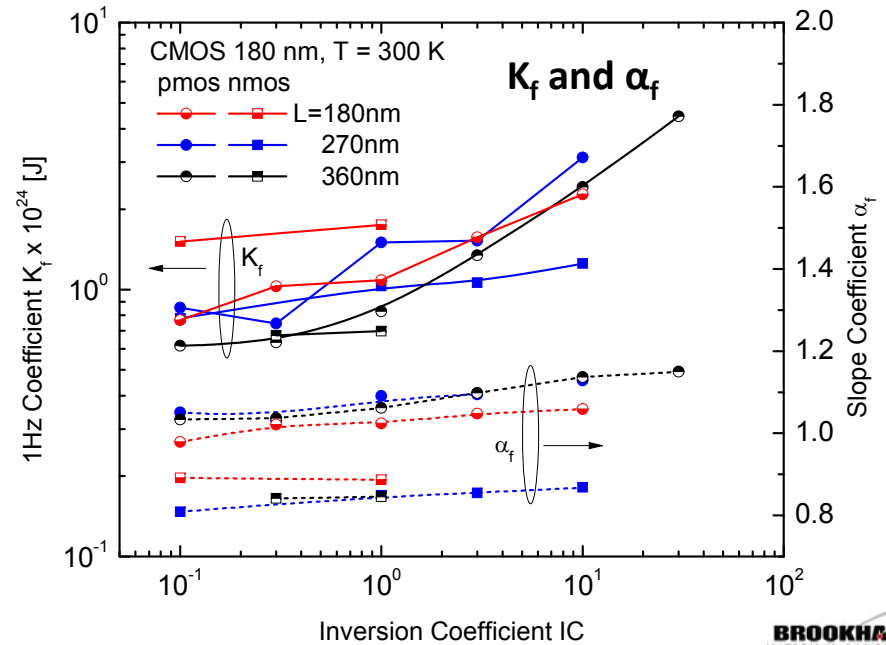- The dependence of  $K_f$  and  $\alpha_f$  on the **operating point** is usually small, more visible in deeper submicron technologies
- Note that:
  - $K_f$  increases with IC
  - also  $\alpha_f$  increases with IC



# The 1/f-equivalent model

 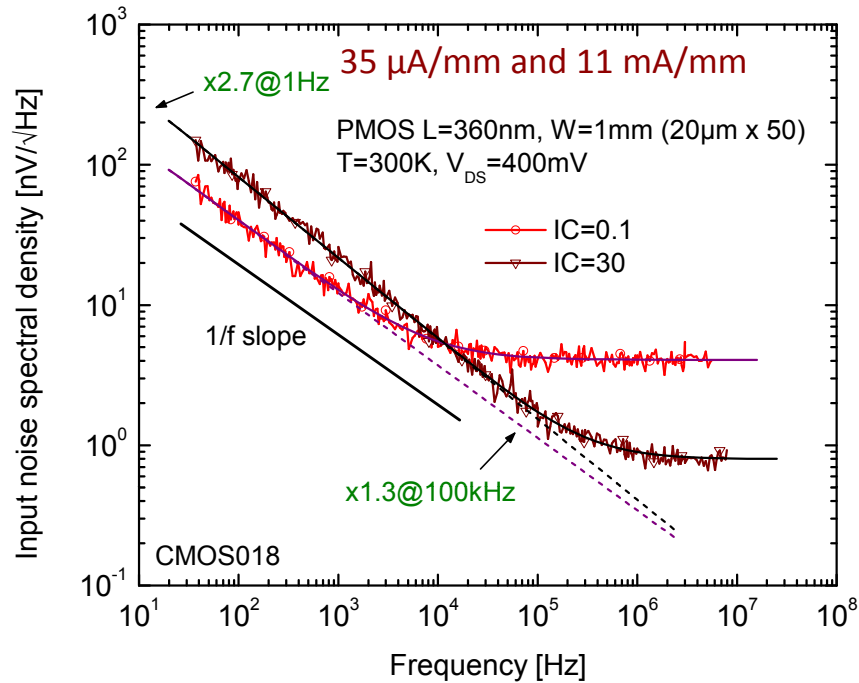


Equivalent 1/f: **equal value at twice the white component** (four times in power)



$$\frac{K_{feq}}{C_{ox} W L f_{eq}} + \text{white} = S_v(f_{eq})$$

where  $S_v(f_{eq}) = 4 \times \text{white}$
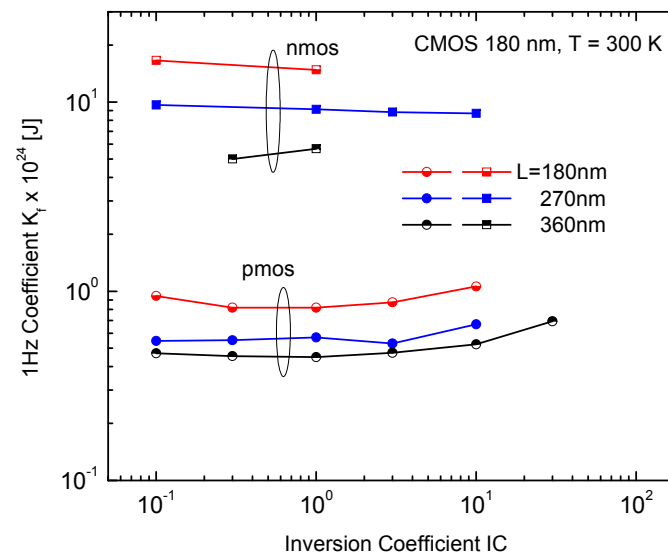
$$\Rightarrow K_{feq} = C_{ox} W L f_{eq} 3 \times \text{white}$$


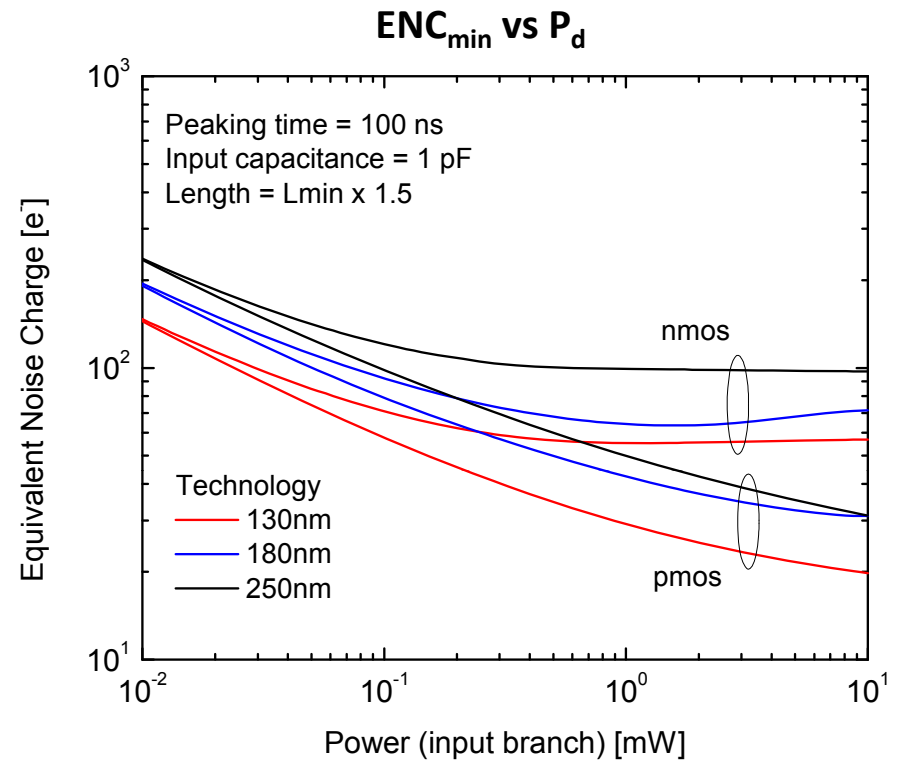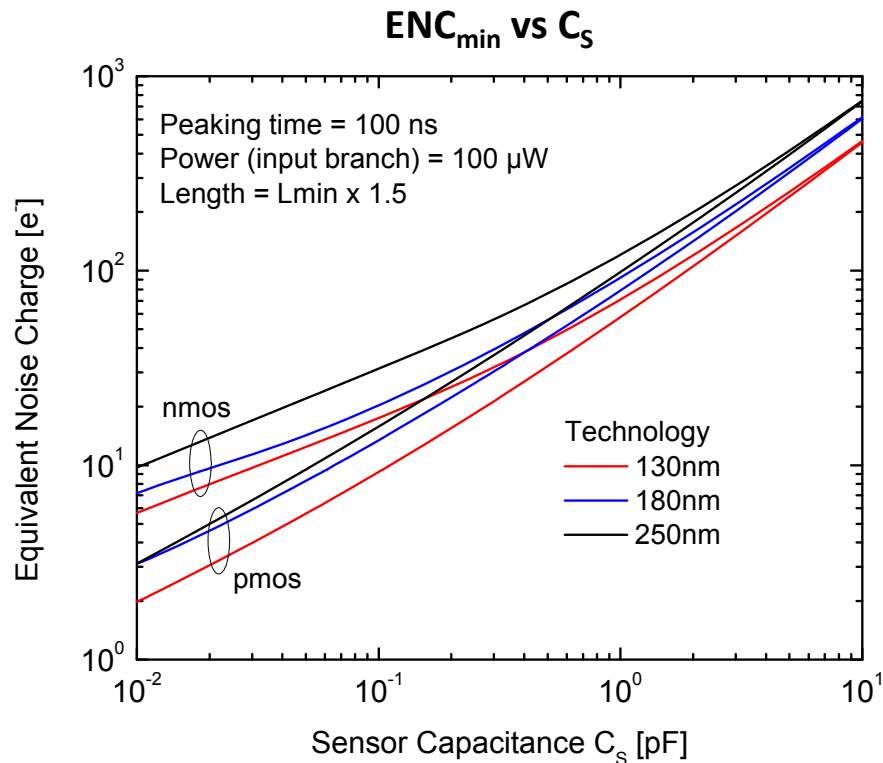
# Example of ENC vs input capacitance and power



- **PMOS** offer typically a better resolution due to higher slope of low-frequency noise.
- **Smaller technology nodes** offer better resolution at equal dissipated power (due to higher drain current from lower voltage).
- The resolution **flattens with power** due to the low-frequency noise. A **minimum** may occur due to increase in capacitance density when entering strong inversion with low-frequency dominant (i.e. nmos).





# Part II

# Amplifier design
 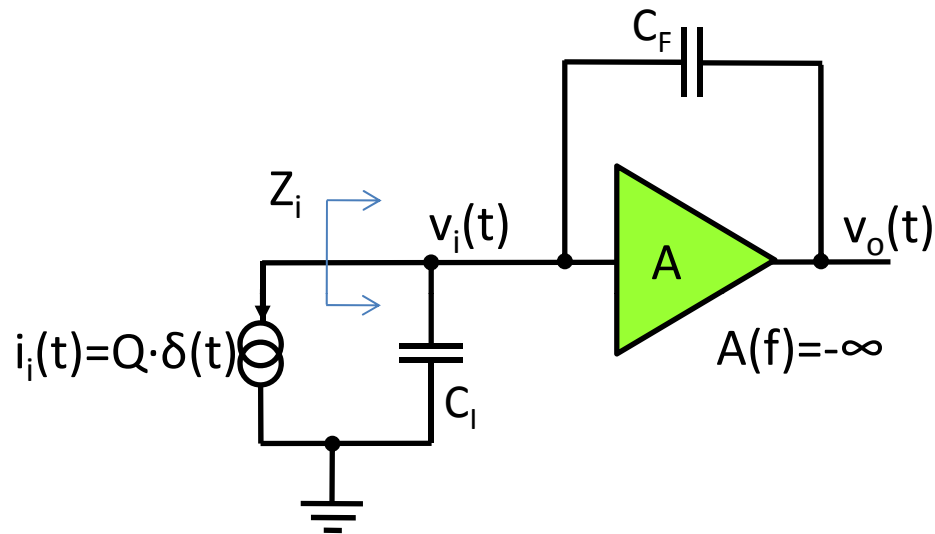
# Charge amplifier response

We start assuming a charge amplifier realized using an **ideal** voltage amplifier with infinite gain and bandwidth, i.e.  $A(f) = -\infty$ .





The response  $v_o(t)$  of the system to a delta current  $\delta(t)$  (area  $Q$ ) is a step, while the input node is steady at the virtual ground. The impedance  $Z_i(f)$  seen by the signal source is zero. The loop gain  $G_L(f)$  is infinite.

$$v_o(t) = \Phi(t) \cdot \frac{Q}{C_F} \quad v_i(t) = 0 \quad Z_i(f) = 0 \quad G_L(f) = \left| A(f) \cdot \frac{C_F}{C_I + C_F} \right| = \infty$$
  
# Constraints on dc gain for charge amplifiers

In a **semi-realistic** case,  $A(f)$  has **finite dc gain**  $-A_0$  and **infinite bandwidth**, i.e.  $A(f)=-A_0$ .



The **response**  $v_o(t)$  of the system to a delta current  $\delta(t)$  (area  $Q$ ) is a step, but attenuated by  $(1+1/G_{L0})$ , while the **input node** is an opposite step,  $A_0$  times smaller.

$$V_o(f) = \frac{Q}{sC_F(1+1/G_{L0})}$$

$$V_i(f) = \frac{V_o(f)}{A(f)} = \frac{-Q}{sC_F A_0 (1+1/G_{L0})}$$

$$G_L(f) = \left| -A_0 \cdot \frac{C_F}{C_I + C_F} \right|$$

$$v_o(t) = \Phi(t) \frac{Q}{C_F(1+1/G_{L0})}$$

$$v_i(t) = -\frac{v_o(t)}{A_0}$$

$$G_{L0} = G_L(0)$$

What is the **impact of low dc gain  $A_0$**  on the front-end performance?

# Constraints on dc gain

The attenuation at  $v_o(t)$  can be recovered by increasing the gain in the next stages, but a low dc gain  $A_0$  can have two relevant effects:

(1) - **Dependence of charge gain on  $A_0$  (i.e. on active elements, temperature, ...).**

We minimize this dependence by increasing the dc loop gain  $G_{L0}$ . As a rule of thumb, a minimum loop gain of 100 should be achieved:

$$G_{L0} = \left| -A_0 \cdot \frac{C_F}{C_i + C_F} \right| > 100$$

(2) - Increase in **cross-talk between channels.**

Assuming an inter-pixel capacitance  $C_C$ , a voltage step at the input injects, at the input of the neighbor channel, a charge:

$$Q_C \approx \frac{Q}{A_0 C_F} C_C$$


We impose

$$Q_{Cmax} \approx \frac{Q_{max}}{A_0} \frac{C_C}{C_F} < ENC$$

i.e.



$$A_0 > \frac{Q_{max}}{ENC} \frac{C_C}{C_F} = DR \frac{C_C}{C_F} \quad \text{Example: } DR \approx 500, C_C/C_F \approx 0.2 \rightarrow A_0 > 100$$

 where  $DR = Q_{max}/ENC$  is the **analog dynamic range**.


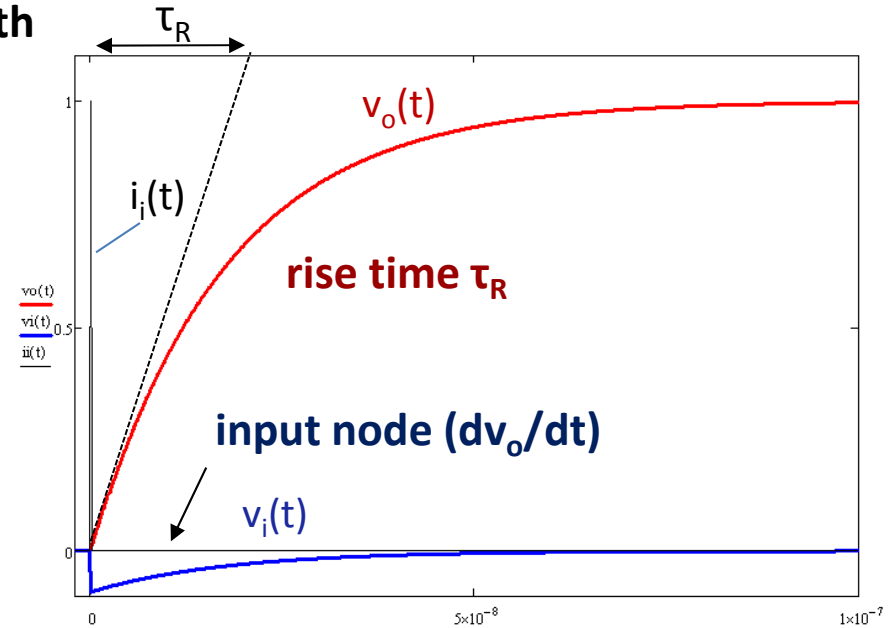 
# Constraints on bandwidth

In a **more realistic** case,  $A(f)$  has **finite bandwidth**



Assuming  $G_{L0} \gg 1$  we can write:

$$V_o(f) \approx \frac{Q}{sC_F} \frac{1}{1 + j2\pi f\tau_R}$$

$$V_i(f) = \frac{V_o(f)}{A(f)}$$

$$\tau_R \approx \frac{\tau_A}{G_{L0}} = \frac{1}{2\pi\text{GBP}} \frac{C_I + C_F}{C_F}$$

$$v_o(t) \approx \Phi(t) \frac{Q}{C_F} \left( 1 - e^{-\frac{t}{\tau_R}} \right)$$

$$v_i(t) \approx -\frac{Q}{C_F A_0} \left[ 1 - \left( 1 - \frac{\tau_A}{\tau_R} \right) e^{-\frac{t}{\tau_R}} \right] \approx -\frac{Q}{C_I + C_F} e^{-\frac{t}{\tau_R}}$$

# Constraints on bandwidth

A low GBP can have two relevant effects:

(1) - **Dependence** of shaped output **on rise time (i.e. on active elements, temperature, ...)**.

We minimize this dependence by increasing the GBP. As a rule of thumb, the rise time should be  $< 0.1 \times$  peaking time:

$$\tau_R < 0.1\tau_P \rightarrow \text{GBP} > \frac{10}{2\pi\tau_P} \frac{C_I + C_F}{C_F}$$

(2) - Increase in **cross-talk between channels**.

Assuming an inter-pixel capacitance  $C_C$ , the additional exponential voltage at the input injects, at the input of the neighbor channel, a current with zero area.

The current generates at the output of the neighbor shaper a signal whose peak amplitude can be approximated with ( $K$  = shaper gain):

$$v_{o2} \approx \frac{QK}{C_F} \frac{\tau_R}{\tau_P} \frac{C_C}{C_I} \approx \frac{QK}{2\pi\text{GBP}\tau_P} \frac{C_C}{C_F^2} \rightarrow Q_{\text{Ceq}} \approx \frac{Q}{2\pi\text{GBP}\tau_P} \frac{C_C}{C_F}$$

We impose

$$Q_{\text{Ceqmax}} < \text{ENC}$$


which gives:

$$\frac{Q_{\text{max}}}{2\pi\text{GBP}\tau_P} \frac{C_C}{C_F} < \text{ENC} \rightarrow \text{GBP} > \frac{\text{DR}}{2\pi\tau_P} \frac{C_C}{C_F}$$

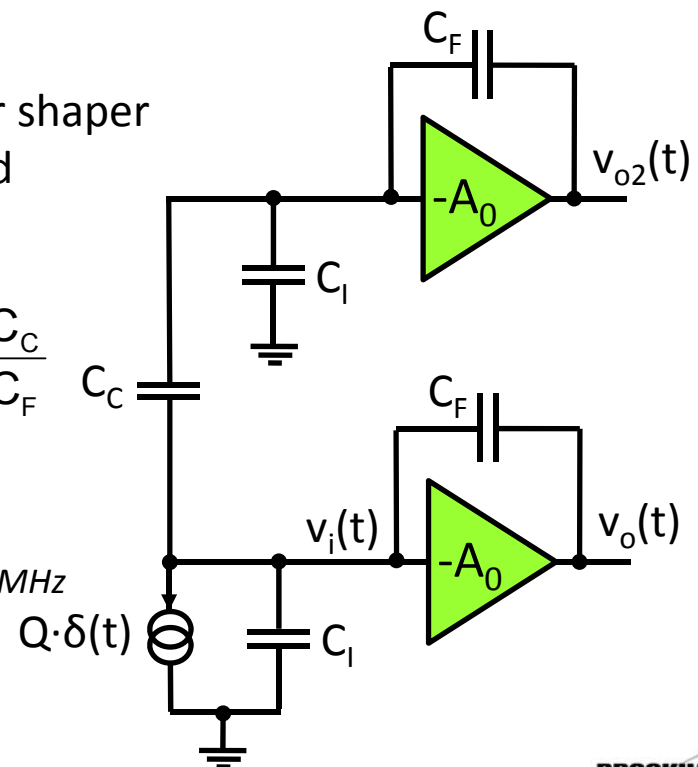Example:



$\text{DR} \approx 500, C_C/C_F \approx 0.2,$

$\tau_P = 100\text{ns} \rightarrow \text{GBP} > 150\text{ MHz}$


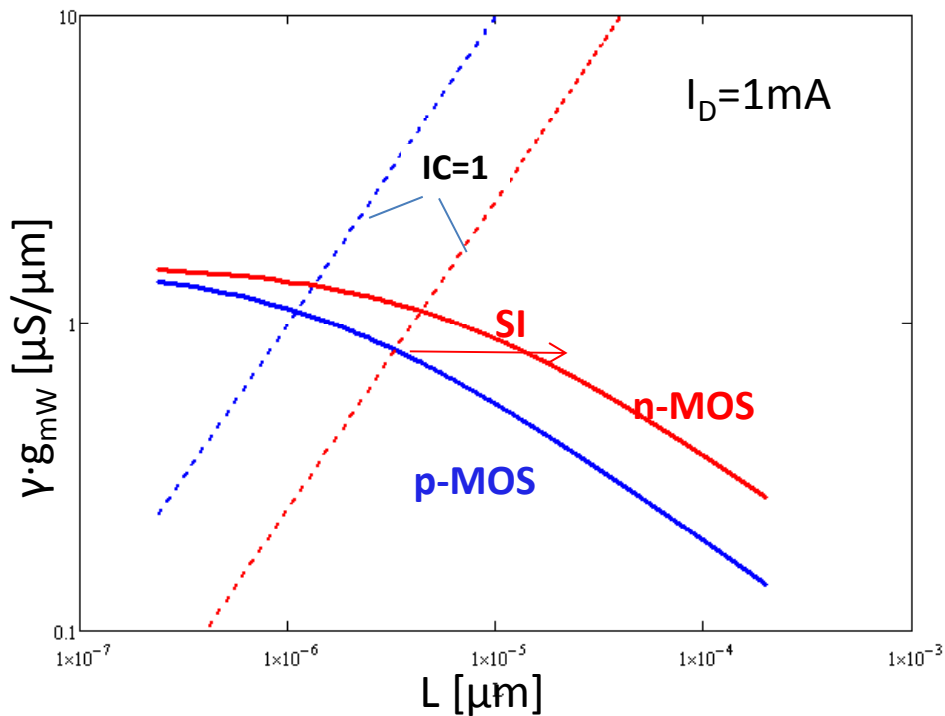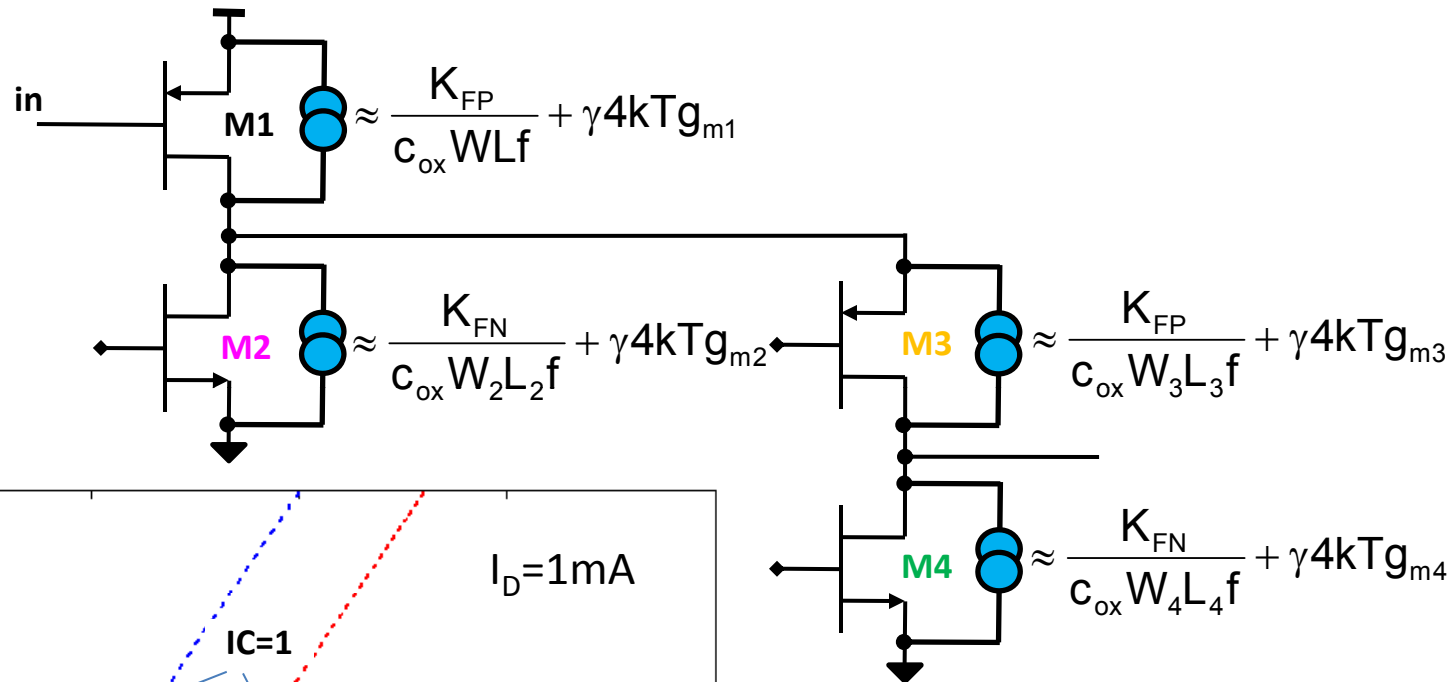
# Noise from current sources

We use **approximate equations** for the noise spectral densities. First we compare the white terms, then the low-frequency terms. Let's start with the **sources M2, M4**.



Observe  $g_m$  vs  $L$  for a given drain current: **the higher the channel length  $L$ , the lower the white noise ( $g_m/I_D$ ).**

In order to minimize the white noise the MOSFET should operate **at the highest possible  $L$  (i.e. strong inversion).**

## Noise from current sources

To achieve this result, we size the load MOSFET for a given  $V_{DS0}$  as follows:

1. **set  $V_{GS}$  at the highest possible value and  $W$  at the minimum value**
2. **increase  $L$  until  $V_{DSAT} = V_{DS0}$  ( $i_{DW}$  is now set)**
3. **increase  $W$  to obtain the desired current  $I_D = i_{DW}W$**

At this point the MOSFET is biased at an inversion as strong as possible, and the **white noise term is minimized**.

Next we **minimize the low frequency term** by increasing both  $L$  and  $W$  while maintaining a fixed  $W/L$  ratio, i.e. a fixed  $g_m$  and operating point (beware of the parasitics!).

The  $W$  and  $L$  are increased until:

$$\frac{K_{F2,4}}{c_{ox} W_{2,4} L_{2,4}} g_{m2,4} \ll \frac{K_{FP}}{c_{ox} WL} g_{m1}$$

Note that, in principle, the low frequency term can be made negligible while the white term cannot.

The higher the available  $V_{DS0}$  (compared with the threshold), the lower the white term.



## Noise from cascode

Concerning the noise contribution from the **cascode  $M_3$** , it is usually negligible.

We can use Blakesley's theorem (assume thermal only):

$$4kTg_{m3} \left( \frac{1-\lambda}{\lambda} \right)^2 \approx 4kTg_{m3} \left( \frac{1}{g_{m3}r_{o1}} \right)^2 \Leftrightarrow \lambda^2 4kTg_{m1}$$

where:  $\lambda = \frac{g_{m3}r_{o1}}{1+g_{m3}r_{o1}} \approx 1$

It follows:

$$\frac{4kT}{g_{m3}} \left( \frac{1}{g_{m1}r_{o1}} \right)^2 \Leftrightarrow \frac{4kT}{g_{m1}}$$


Note that  $r_{o1}$  must be **compared with**  $\frac{C_i}{g_{m1}C_{gd}}$ , whichever is the lowest:

$$\frac{4kT}{g_{m3}} \left( \frac{C_{gd}}{C_i} \right)^2 \Leftrightarrow \frac{4kT}{g_{m1}}$$


We conclude that  **$M_3$**  should have the **minimum L** (maximum  $g_m$ ) while the width  $W$  is set as a trade-off between the dc gain and the secondary pole at the source of  $M_3$ .

Note also that the **resistance at the drain** of  $M_1$  is (cascode efficiency):
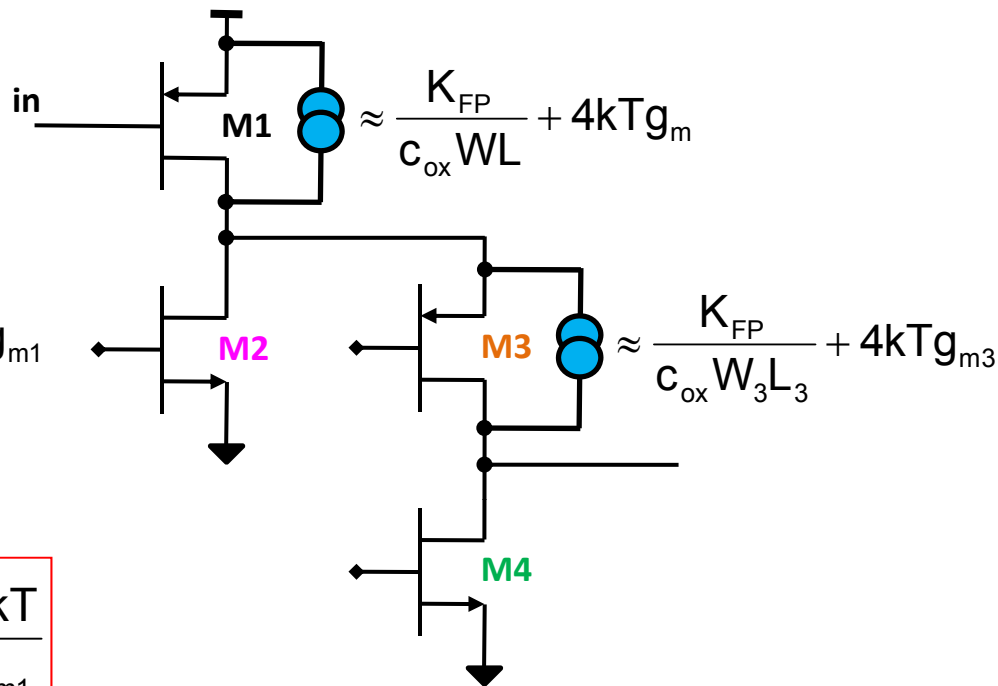
$$r \approx r_{o1} \frac{r_{o4} + r_{o3}}{r_{o4} + r_{o3} (1 + g_{m3}r_{o1})} \approx \begin{cases} \frac{r_{o1}}{1 + g_{m3}r_{o1}} \approx \frac{1}{g_{m3}} & \text{small } r_{o4} \\ r_{o1} & \text{large } r_{o4} \quad (\text{more realistic}) \end{cases}$$




# Cascoding for large input capacitance

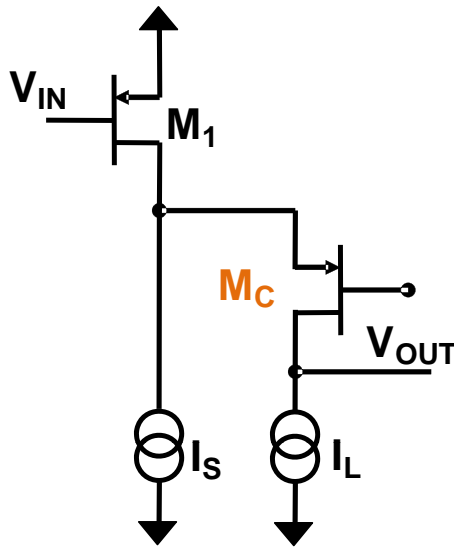


single cascode

 Issues: dc gain, secondary pole, charge gain



amplified cascode

 


dual cascode

- + cascode impedance reduced by  $M_A$  gain
- + adds third pole, but both poles are at high freq.
- ± additional voltage drop set by threshold of  $M_A$
- requires additional power (noise from  $M_A$ )
- real poles if:

$$g_{mA} > 4g_{mC} \frac{C_{gd1} + C_{gsA}}{C_{gdA} + C_{gsC}}$$

- + cascode impedance reduced through  $M_D$
- + add third pole, but both poles are at high freq.
- ± additional voltage drop controlled by bias circuit
- + does not require additional power
- + always real poles
- + optimum size  $\approx 1/3$  to  $1/4$  of  $M_1$
- slightly higher node resistance

# Rail-to-rail voltage amplifier

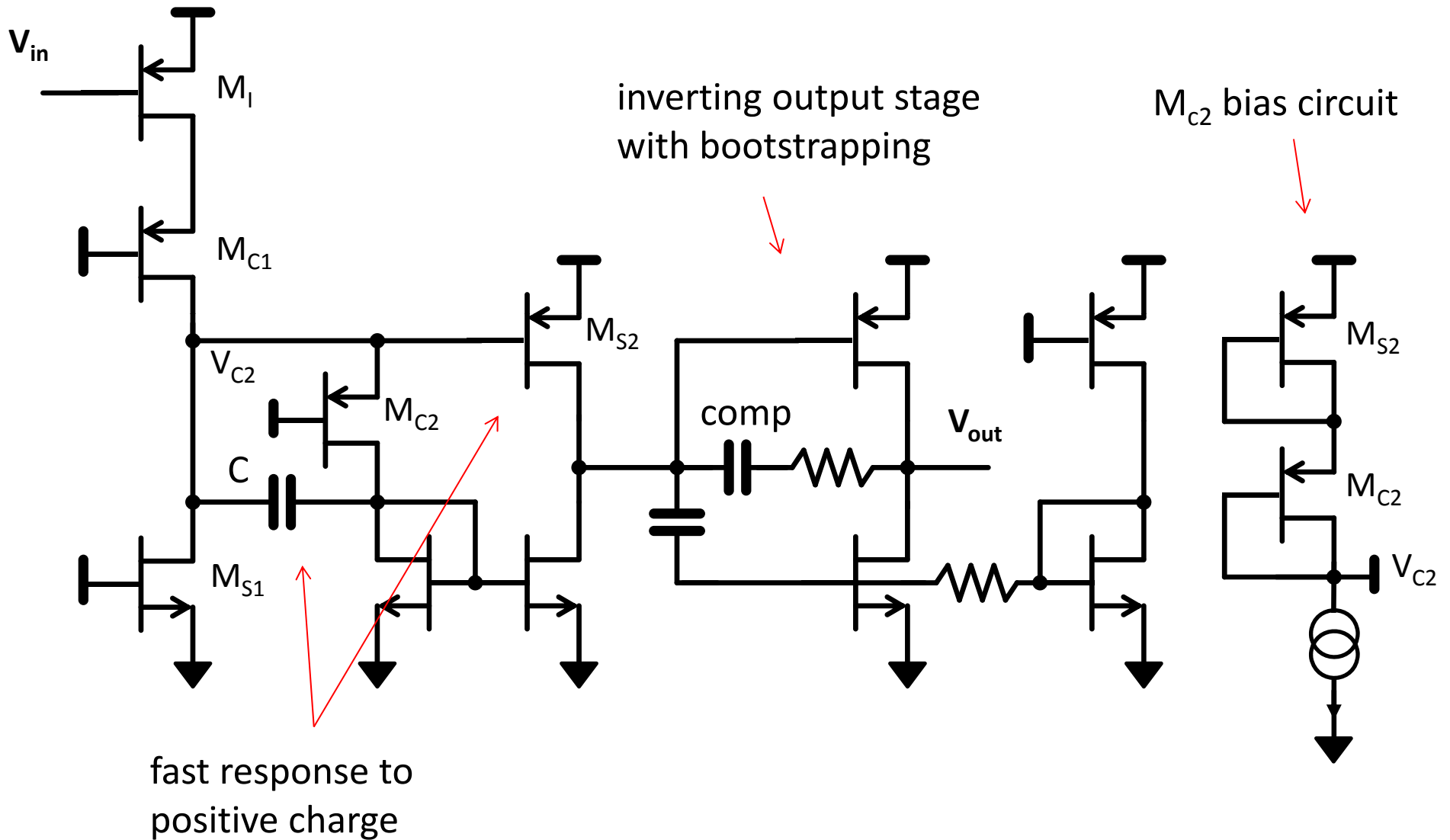


## Part III

# Charge amplification
 
# Charge amplifier


A charge amplifier, in its **classical definition**, is composed of a voltage amplifier **A** and a feedback capacitor  $C_F$ . The **capacitor integrates** the current  $Q \cdot \delta(t)$  released by the sensor. It provides a “**virtual ground**” at the input node, thus stabilizing the potential of the sensor electrode along with providing **low-noise charge-to-voltage conversion**.





Charge amplifiers require an additional low-frequency **network R** (known as “**reset**”) in feedback for (i) stabilization of the bias point and (ii) discharge (continuous or switched) of the feedback capacitor  $C_F$ . A **properly designed reset** has negligible effect on the signal processing ( $R$  is very large) and, in most cases, little effect on the resolution.
 
# Adaptive continuous reset

$L/W \gg 1$ , strong inversion, saturation




 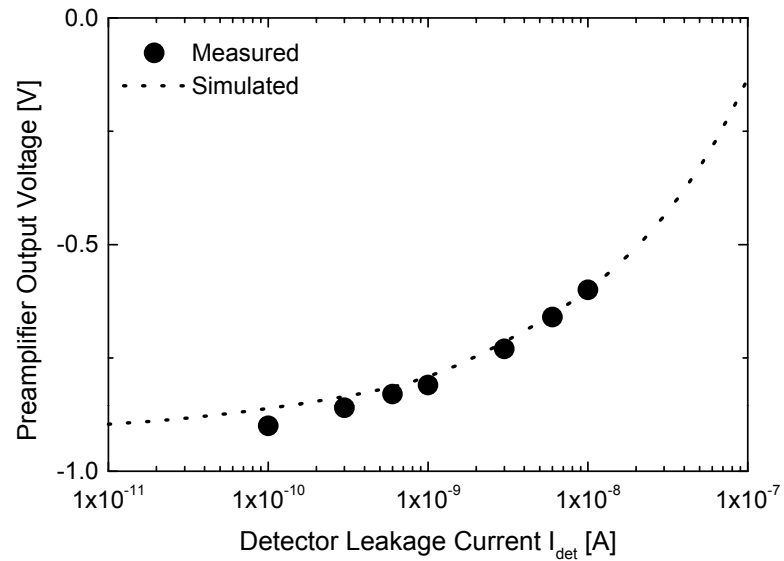shot noise equivalent:  $4kT/R = 2qI_{eq}$



# Compensated adaptive reset: charge amplification

$\sim 100 e^-$  at 100ns !

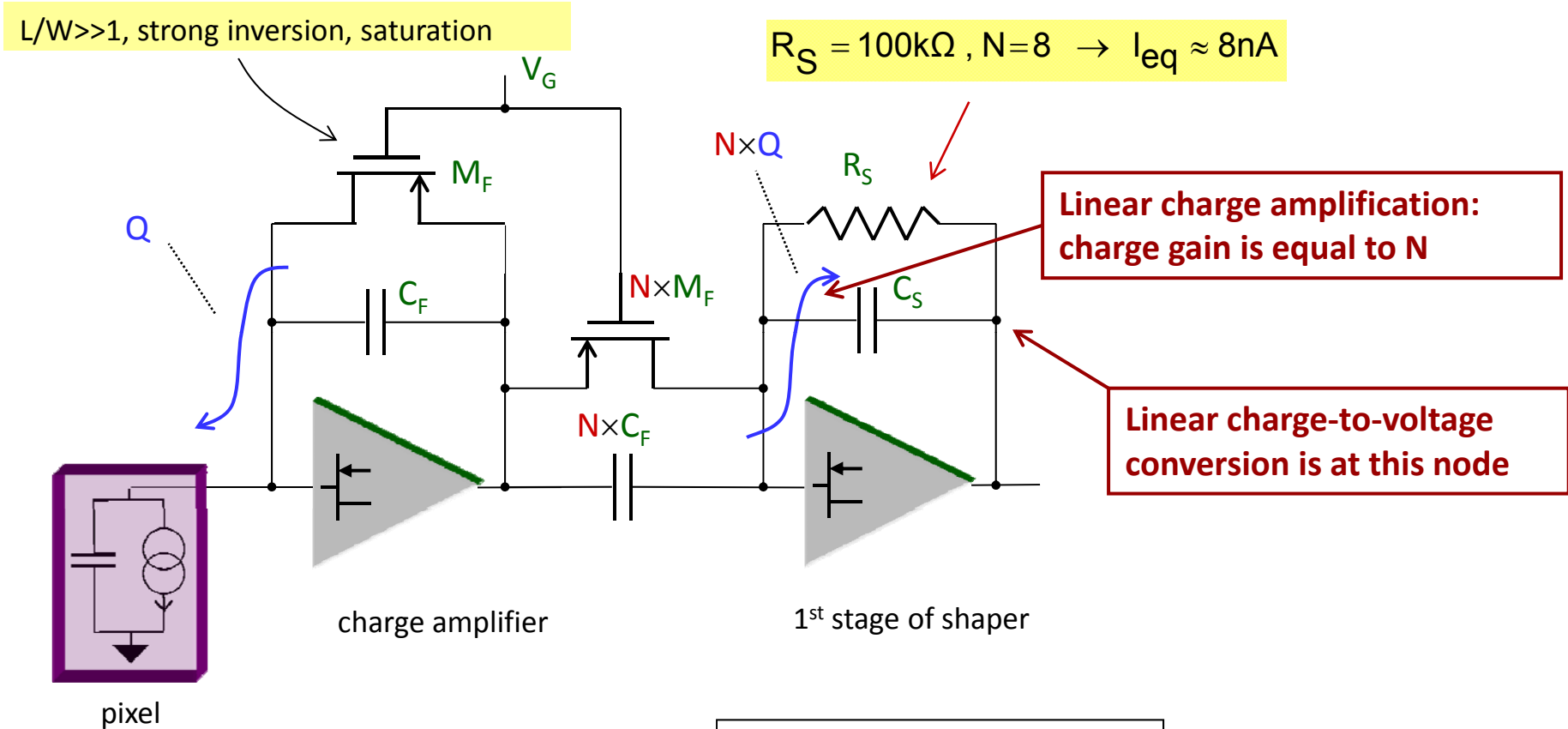

- Charge gain  $N$
- High linearity (charge)
- Low noise
- Adaptive


G. De Geronimo et al., IEEE TNS 47 (2000)

# Doubling the reset

$\sim 11 e^-$  at 100ns !

$R_S = 100k\Omega, N \times N_2 = 64 \rightarrow I_{eq} \approx 100pA$

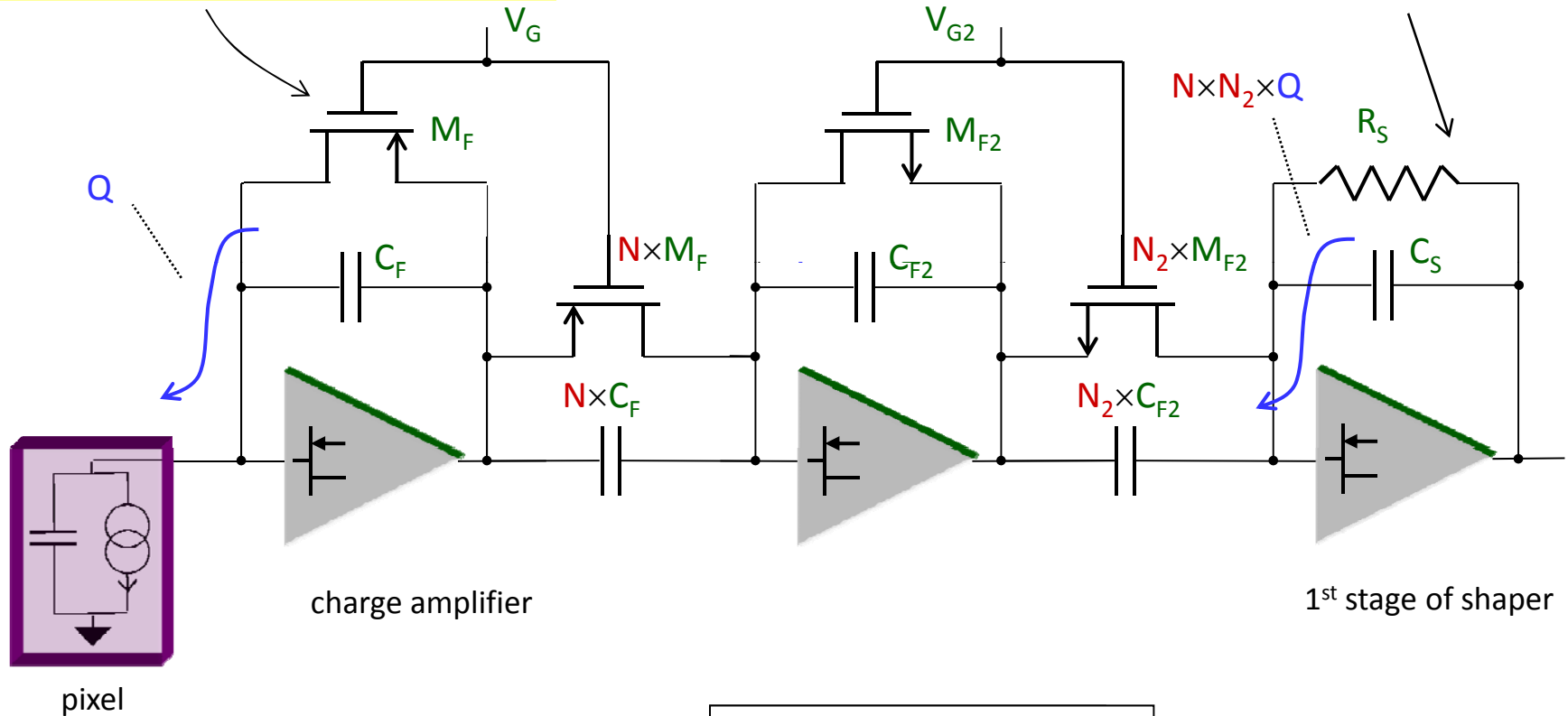
$L/W \gg 1$ , strong inversion, saturation



- Charge gain  $N \times N_2$
- High linearity (charge)
- Low noise
- Adaptive
- Limited swing



# Low-voltage configuration

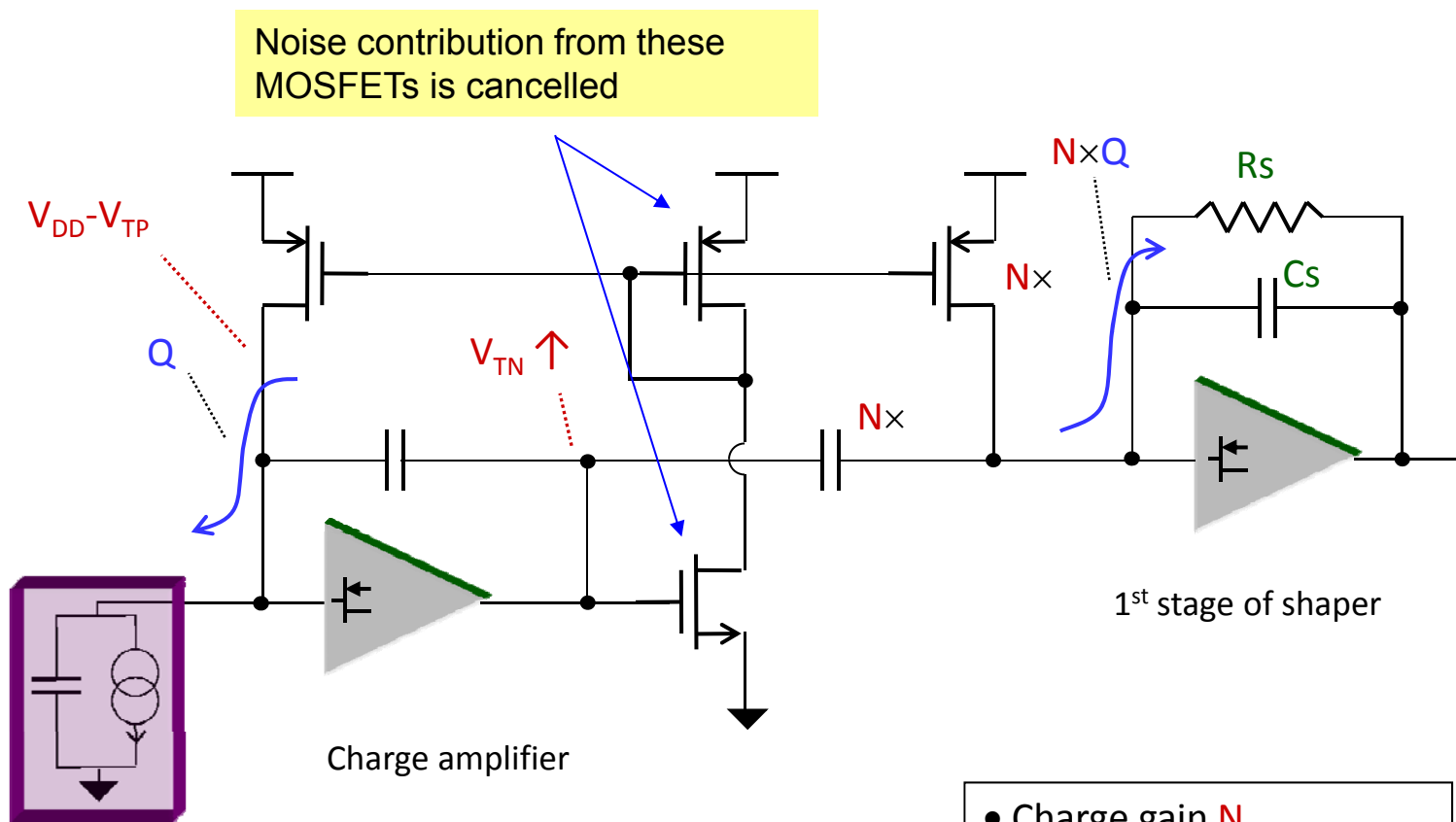

- Charge gain  $N$
- High linearity (charge)
- Low noise
- Adaptive
- High swing


G. De Geronimo et al., IEEE TNS 54 (2007)

**Part IV**

**Filter design**

**(analog dynamic range)**

# Maximum charge

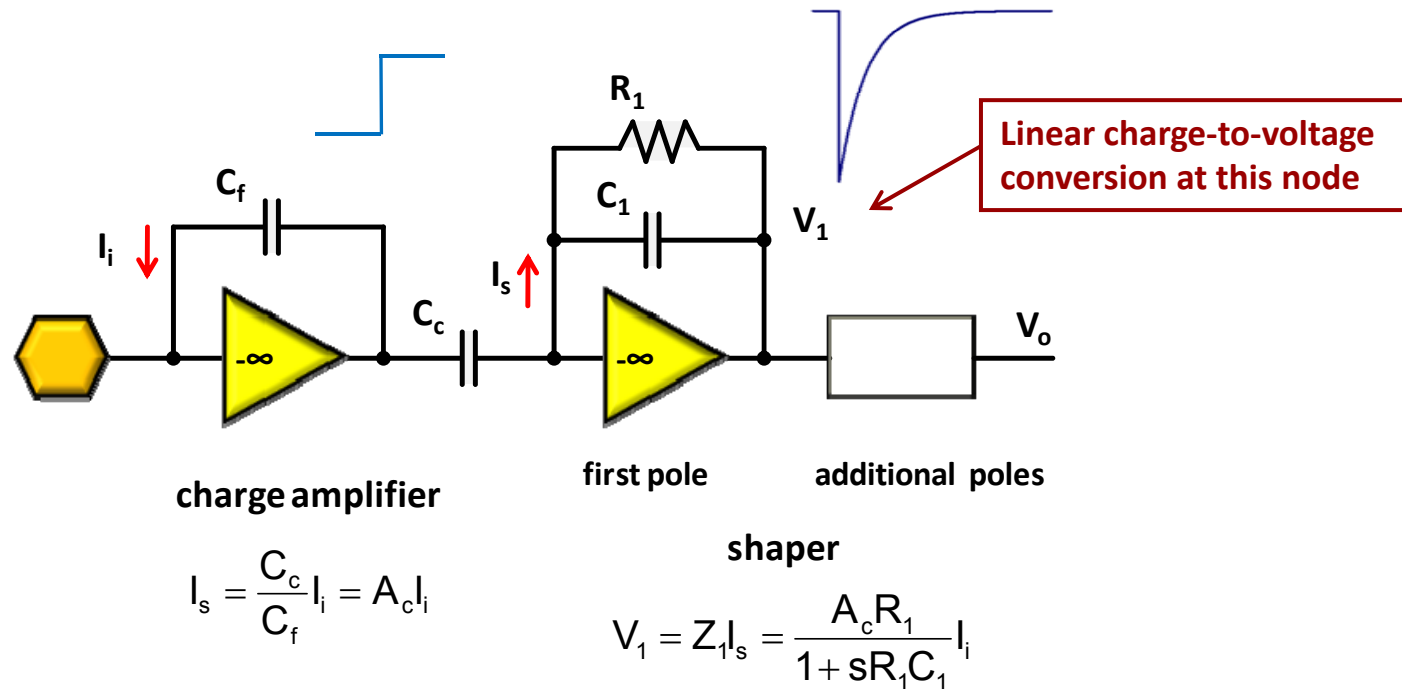

The **voltage linearity at the output node of the charge amplifier is not required**, as long as the desired linear charge amplification  $A_c = C_c / C_f$  is achieved at  $v_o$ .


However, the **outputs of the filtering stages (e.g.  $v_1$ ) must be linear**.

The **maximum charge** can be calculated as

$$Q_{\max} = \frac{C_1 V_{1\max}}{A_c}$$

**Given a maximum charge  $Q_{\max}$  we must select  $A_c$ ,  $C_1$  and  $V_{1\max}$**

## Shaper noise

 


The contribution to the ENC from the noisy (i.e. dissipative) element  $R_1$  can be calculated from the **equivalent parallel noise at the input**

$$ENC_{s1}^2 = \frac{A_{iwp}}{A_c^2} \frac{4kT}{R_1} \tau_p = \frac{A_{iwp}}{A_c^2} \frac{4kT}{R_1} \eta_p R_1 C_1 = A_{iwp} \eta_p 4kT \frac{C_1}{A_c^2}$$

The ratio  $\eta_p = \tau_p / R_1 C_1$  is defined by the type of filter (shaper).

Typically  $A_{iwp} \eta_p \sim 1$  to 2.

# Analog dynamic range

 

The **analog dynamic range** is defined as

$$DR = \frac{Q_{\max}}{\sqrt{ENC_{ca}^2 + ENC_{s1}^2}}$$

The design proceeds with the following steps:

- 1) Maximize the front-end resolution (minimize  $ENC_{ca}$ )
- 2) Optimize dynamic range (**minimize  $ENC_{s1}$** )

$$DR = \frac{Q_{\max}}{\sqrt{ENC_{ca}^2 + ENC_{s1}^2}} = \frac{Q_{\max}}{\sqrt{\rho \cdot ENC_{s1}^2}} \quad \rho = \frac{ENC_{ca}^2 + ENC_{s1}^2}{ENC_{s1}^2}$$

we must set the value of the coefficient  $\rho (>1)$

# Optimizing the dynamic range

$$DR \approx \frac{Q_{\max}}{\sqrt{\rho \cdot ENC_{s1}^2}} = \frac{\frac{C_1 V_{1\max}}{A_c}}{\sqrt{\rho \cdot \frac{A_{iwp} \eta_p}{A_c^2} 4kTC_1}} = \frac{V_{1\max} \sqrt{C_1}}{\sqrt{4kT\rho \cdot A_{iwp} \eta_p}}$$

- DR is proportional to  $V_{1\max}$  → use **rail-to-rail**
- DR does not depend on the peaking time  $\tau_p$  or resistor  $R_1$
- $\rho$  is a **key design parameter** (which defines  $C_1$  and  $A_c$  for a given  $Q_{\max}$ )  $Q_{\max} = \frac{C_1 V_{1\max}}{A_c}$


The dynamic range can be increased (i.e.  $A_c$  decreased) at the expense of the ENC.

Values of  $\rho$  **lower than 1.1** (ENC dominated by  $ENC_{s1}$ ) would **not benefit much the DR but would further limit the resolution** by increasing the total ENC ( $\rho$  cannot be lower than 1).

Values of  $\rho$  **higher than 30** (ENC dominated by  $ENC_{ca}$ ) would **not benefit much the ENC but would further limit the DR**.





A convenient choice is  $\rho \approx 5.76$  where  $ENC_{s1}$  contributes to the rms at 10% ( $ENC_{s1}/ENC_{ca} \approx 0.46$ ).

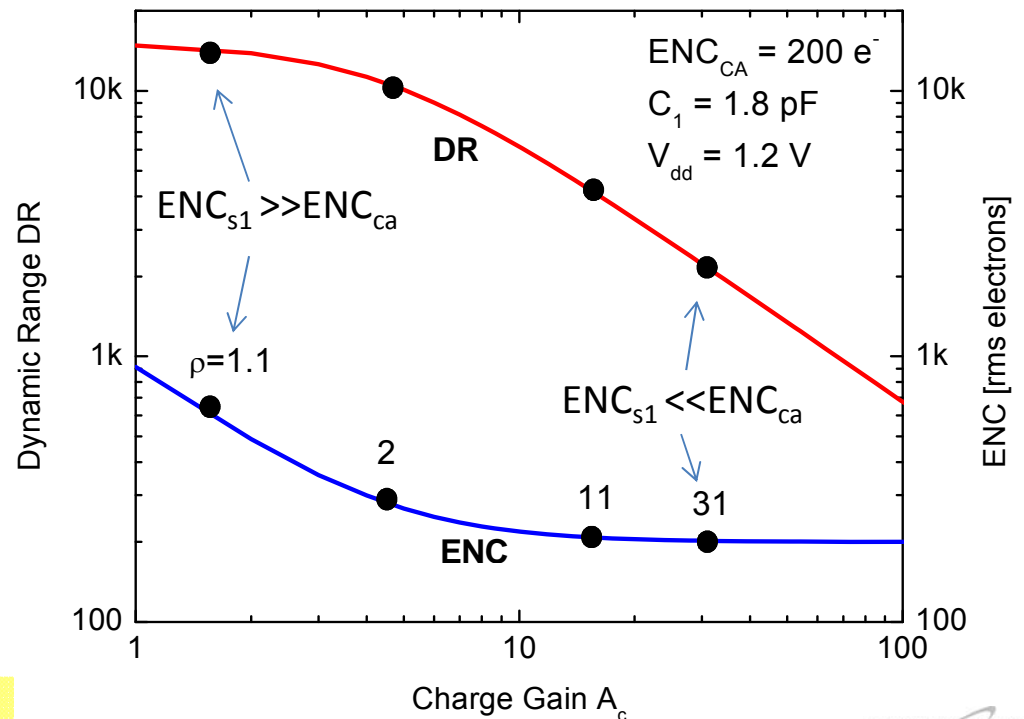*Example: CMOS 130nm (1.2V), 1.8pF, → DR ~ 6,000*



Can we decrease  $\eta_p = \tau_p / R_1 C_1$  ?

# Scaling R with mirrors

    

Noise contribution from R:  $S_{nR} = \frac{4kT}{\lambda R_{eq}}$


Noise **contribution from M<sub>F</sub>** (imposing linearity with  $g_{mR}R \gg 1$ ):  $S_{nMF} = 2qI_F = \frac{2qI_R}{\lambda} \gg \frac{2qnV_T}{R\lambda} = \frac{2kT}{R_{eq}}$

Signal through active components affect **linearity** and introduce **non-stationary noise**  $S/N \sim \sqrt{N_e A_c}$
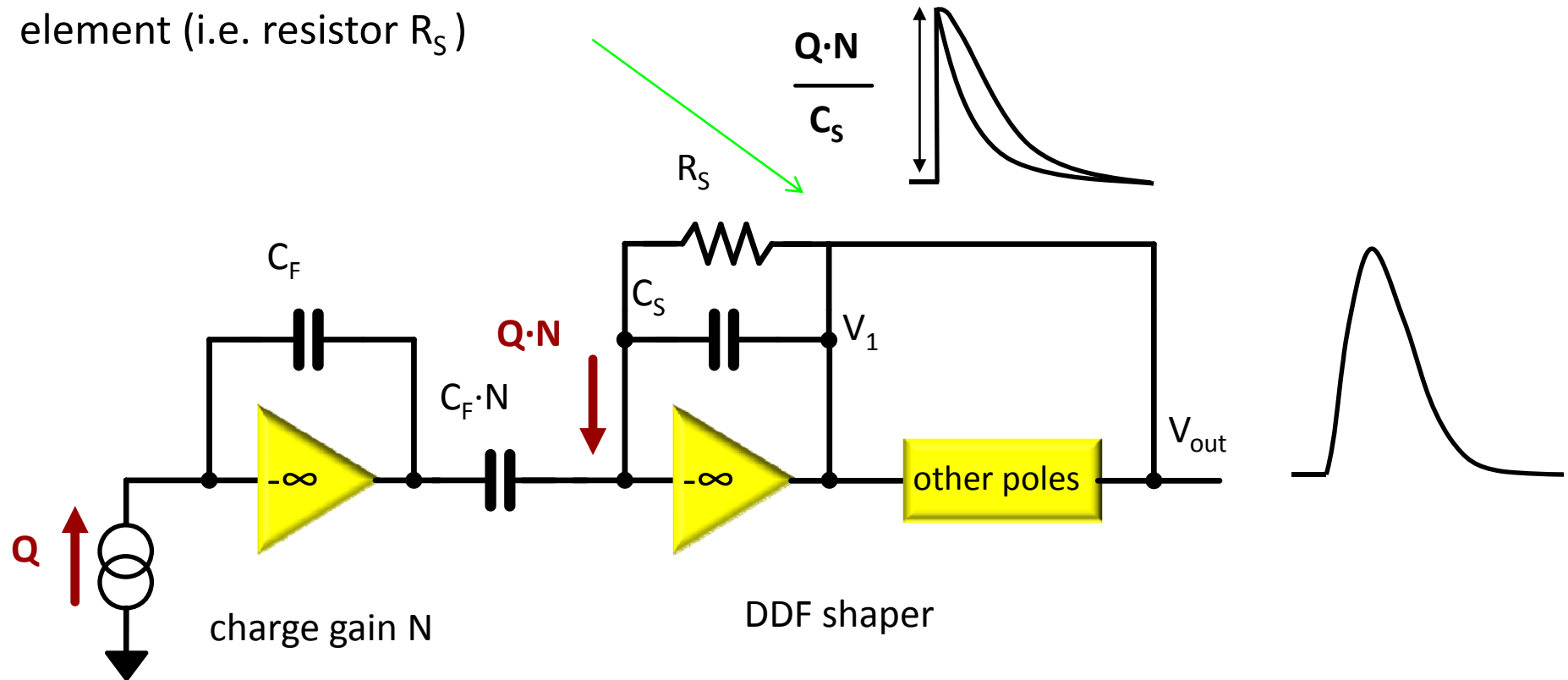
# Delayed Dissipative Feedback (DDF)



delay feedback of dissipative element (i.e. resistor  $R_S$ )



higher analog dynamic range

Applies also to the other stages of the shaper  
see G. De Geronimo and S. Li, TNS 58, Oct. 2011



$$DR_a = \frac{Q_{\max}}{\sqrt{ENC_{CA}^2 + ENC_S^2}}$$





# Delayed Dissipative Feedback (DDF)




Classical

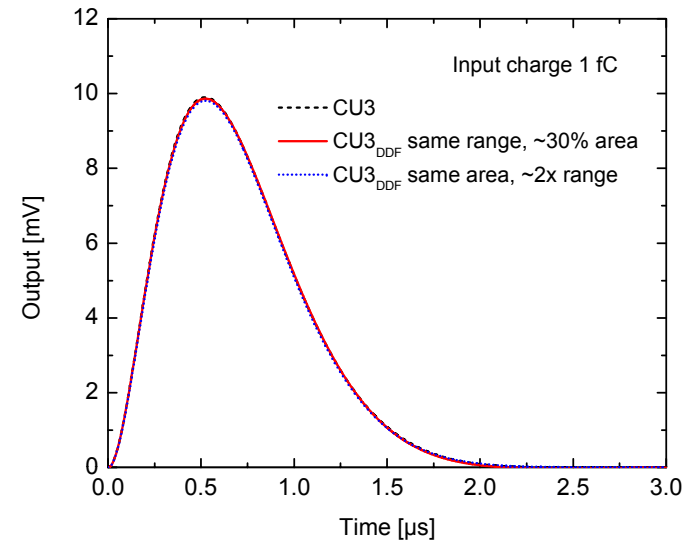 

DDF equal DR

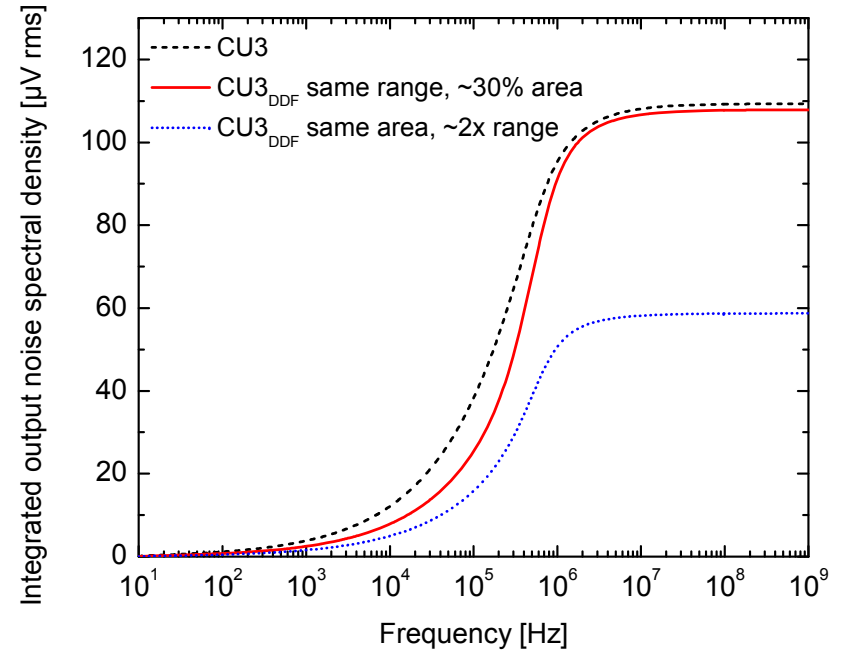 

DDF equal C

 

Example: CMOS 130nm (1.2V), 1.8pF, → DR ~ 12,000

G. De Geronimo et al., IEEE TNS 58 (2011)

Higher dynamic range in limited area requires **multi-range** or **charge subtraction** techniques

# Summary

## I. Input MOSFET optimization

- model and operation in moderate inversion
- low-frequency noise and  $1/f$  equivalent
- resolution vs technology

## II. Amplifier design

- rules of thumb for gain and bandwidth
- dealing with secondary noise sources
- advanced cascoding

## III. Charge amplification

- charge gain and adaptive continuous reset

## IV. Filter design

- impact on analog dynamic range
- optimization : area and voltage
- delayed dissipative feedback (DDF)

# Backup slides

# ENC ( $\tau_p$ ) coefficients for most common filters

Filter	Shape	$a_w$	$a_f(1)$	$a_p$	$\rho_f(\alpha_f)=a_f(\alpha_f)/a_f(1)$	$\tau_w/\tau_p$
RU-2		0.92	0.59	0.92		7.49
RU-3		0.82	0.54	0.66		5.04
RU-4		0.85	0.53	0.57		4.17
RU-5		0.89	0.52	0.52		3.72
RU-6		0.92	0.52	0.48		3.46
RU-7		0.94	0.51	0.46		3.28
CU-2			0.93	0.59		0.88
CU-3	0.85		0.54	0.61	3.92	
CU-4	0.91		0.53	0.51	3.16	
CU-5	0.96		0.52	0.46	2.84	
CU-6	1.01		0.52	0.42	2.66	
CU-7	1.04		0.52	0.40	2.55	
RB-2			1.03	0.75	1.01	
RB-3		1.11	0.78	0.76	9.87	
RB-4		1.30	0.81	0.66	7.67	
RB-5		1.47	0.85	0.62	6.61	
RB-6		1.61	0.87	0.59	5.96	
RB-7		1.74	0.90	0.57	5.53	
CB-2			1.08	0.80	1.02	
CB-3	1.27		0.86	0.76	7.29	
CB-4	1.58		0.93	0.67	5.58	
CB-5	1.87		0.98	0.62	4.80	
CB-6	2.10		1.03	0.60	4.39	
CB-7	2.33		1.06	0.57	4.10	

R = real coincident poles, C = complex-conjugate poles, U = unipolar, B = bipolar

## FET parasitic resistances

Consider the four parasitic resistors  $R_{GG}$ ,  $R_{BB}$ ,  $R_{SS}$ , and  $R_{DD}$ , each contributing with thermal noise. These parasitic resistors come mainly from the physical layout. Assume that the resistor values are low enough to have no impact on the signal response. Assume for simplicity a low impedance at the drain.

Let's analyze the noise contributions compared to the FET channel's white noise  $\approx 4kTg_m$ .


Assuming a large output resistance the relative contribution from  $R_{DD}$  is negligible (use Blakesley to verify).

The relative contribution from  $R_{SS}$  in the frequency range within  $f_T$  can be approximated with:

$$\frac{4kT}{R_{SS}} \left( \frac{R_{SS}g_m}{1 + R_{SS}g_m} \right)^2 \approx 4kTR_{SS}g_m^2 \Leftrightarrow 4kTg_m$$

and it can be made negligible if  $R_{SS} \ll \frac{1}{g_m}$

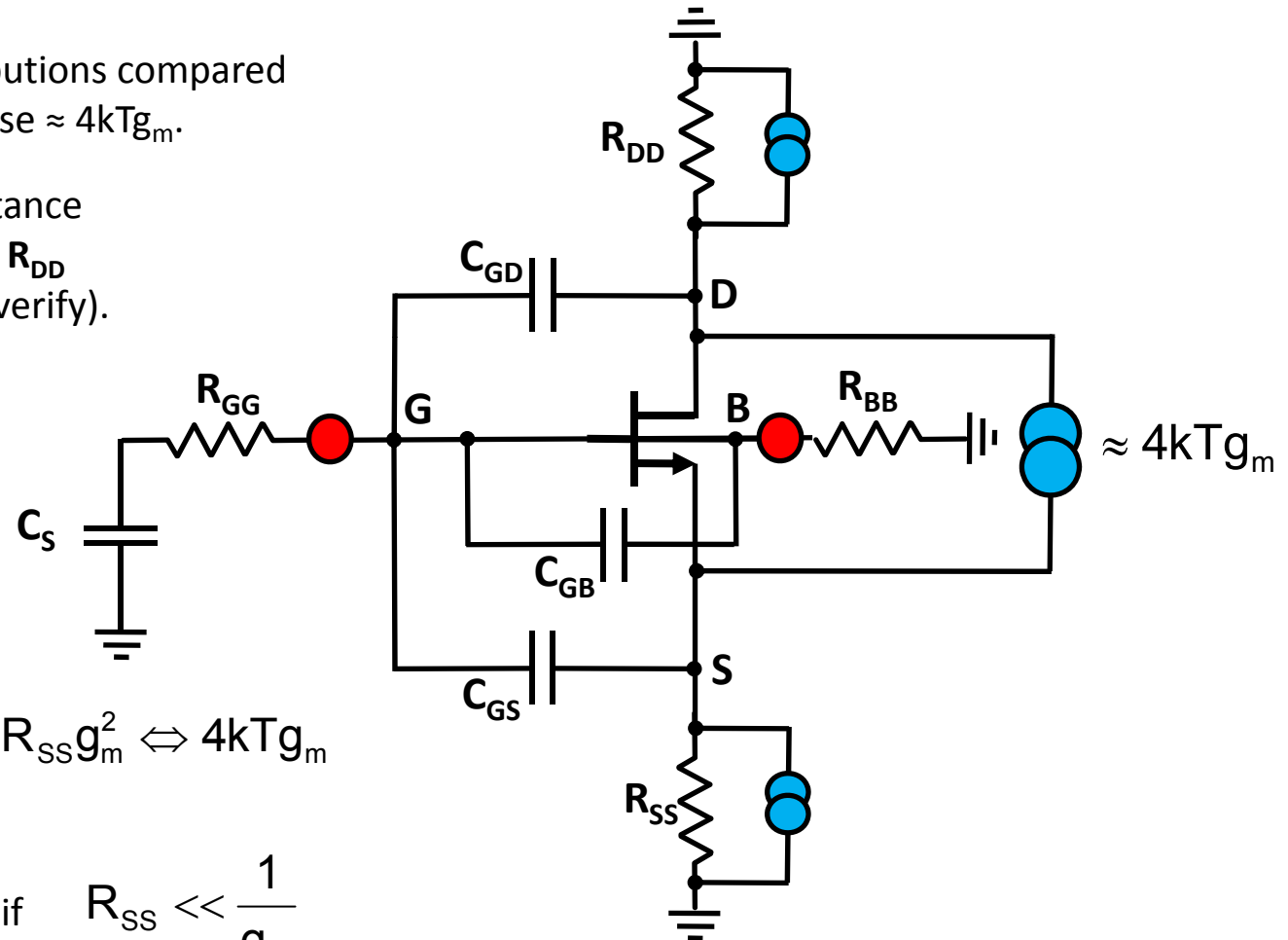which can be obtained in the layout by **increasing the Source diffusion size, its number of contacts, and the width of the interconnection.**



# FET parasitic resistances

The gate and bulk parasitic resistors require more attention.


Let's consider first the contribution from  $R_{GG}$ .

With arguments similar to the base spreading resistance in the BJT, the relative contribution from  $R_{GG}$  can be approximated as:

$$4kTR_{GG}g_m^2\gamma_{GG}^2\lambda \Leftrightarrow 4kTg_m$$

$$\gamma_{GG} = \frac{C_S}{C_S + C_G}$$
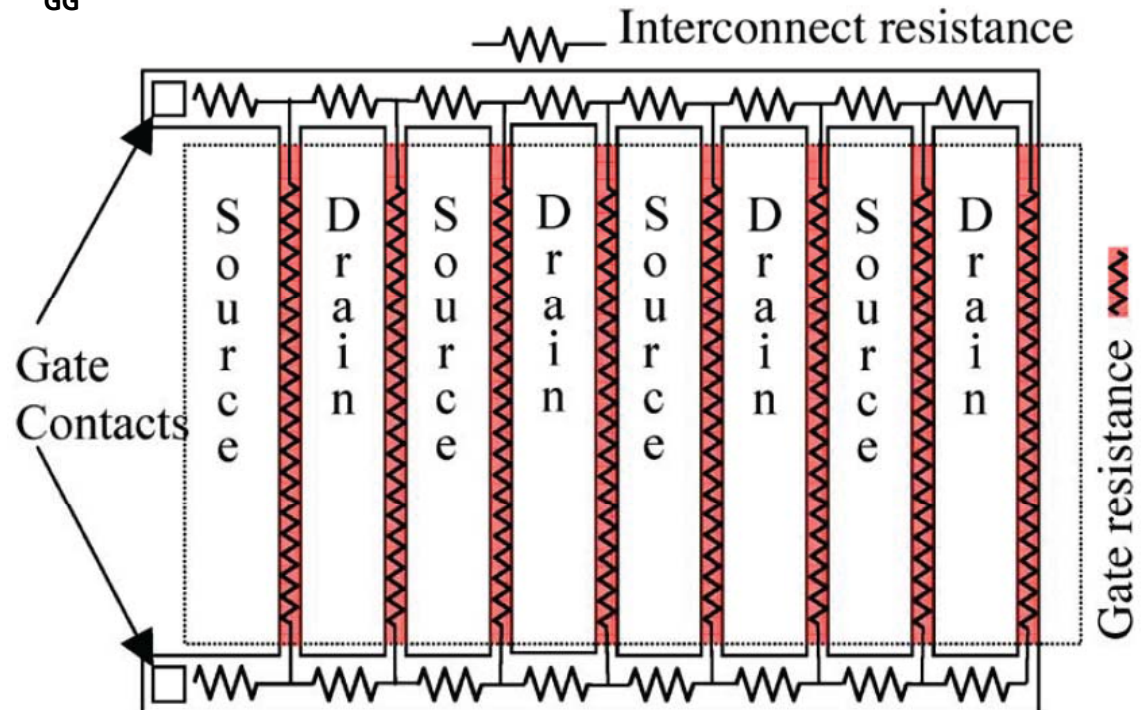
$$\lambda \approx \begin{cases} 1/3 & \text{single side gate contact} \\ 1/12 & \text{dual side gate contact} \end{cases}$$



The  $R_{GG}$  contribution can be made negligible if  $R_{GG} \ll \frac{1}{g_m\gamma_{GG}^2\lambda}$

which can be obtained in the layout by **increasing the number of fingers**.

Note: the interconnect resistance can be made negligible with contacts and metals.

Ref: R. P. Jindal, "Compact noise models for MOSFETs", IEEE TED 53, pp. 2051-2061, 2006

# FET parasitic resistances

Finally let's consider the contribution from  $R_{BB}$ .

This contribution can be non negligible, especially in technologies that use epitaxial layer, which is characterized by a resistivity higher than the substrate. The relative contribution from  $R_{BB}$  can be approximated as:

$$4kTR_{BB}g_{mB}^2 \Leftrightarrow 4kTg_m$$

and it can be made negligible if  $R_{BB} \ll \frac{g_m}{g_{mB}^2} = \frac{1}{g_m(n-1)^2}$

which can be partially obtained by minimizing the distance between the channel and the guard ring diffusion:

- making the layout more rectangular than square by **increasing the number of fingers**;
- **extending the guard ring diffusion** as close as possible to the channel

Note: the limit in the number of fingers is set by the real estate and parasitic capacitances at the gate and drain

Example of layout

