



Discriminator design

Angelo Rivetti
INFN-Sezione di Torino
rivetti@to.infn.it



Comparator generals




- **A comparator discriminates a good event against noise**
- **Comparators are particularly critical in timing systems**

- **Type of comparators:**
 - **General purpose, low power leading edge**
 - **Fast (multi-stage) leading edge**
 - **Latched comparators**
 - **Timing comparators**
 - **Zero crossing**
 - **Constant Fraction**



Leading edge discriminators



 
- High gain, open-loop, **differential amplifiers**.
- **Essential** elements also of the **more complex** zero-crossing and CFD discriminators.
- Should generate logic valid signal from a difference between the inputs as small as possible.



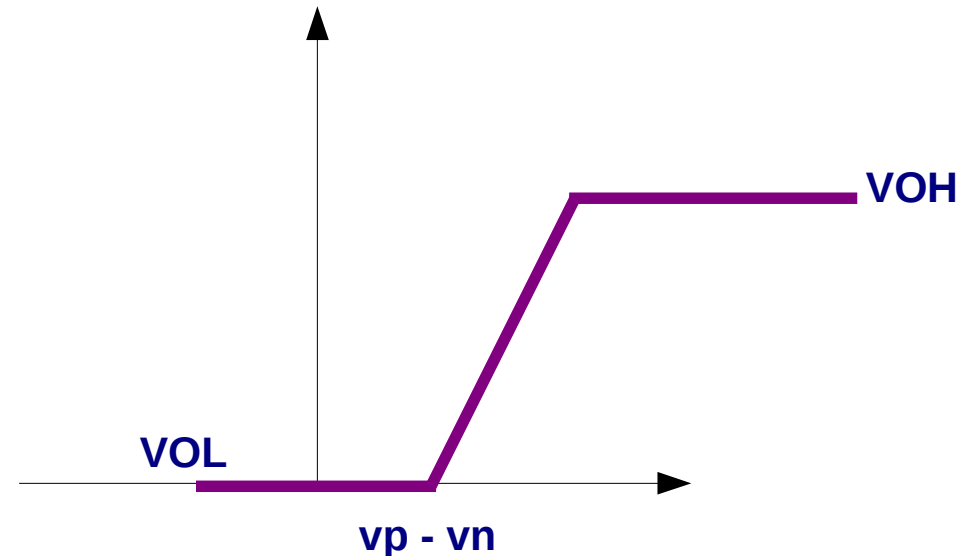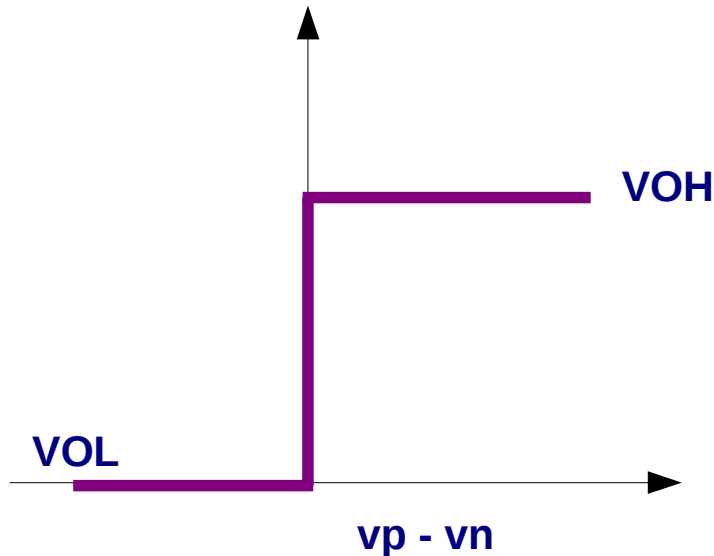- Offset is due to transistor mismatch always affect discriminators (effective threshold change)
- Offset need to be corrected for. Very often this is achieved with Digital to Analog (DAC) converters.
- Propagation delay: time needed for the output to reach 50% measured with respect to the threshold crossing.



Discriminator propagation delay

 

$$A(s) = \frac{A_0}{(1 + s\tau_p)}$$

$$\frac{V_{OH} - V_{OL}}{2} = V_{in(min)} A_0 (1 - e^{-\frac{t_d}{\tau_p}})$$

$$V_{in(min)} = \frac{V_{OH} - V_{OL}}{A_0}$$

$$\frac{V_{OH} - V_{OL}}{2} = \frac{V_{OH} - V_{OL}}{A_0} A_0 (1 - e^{-\frac{t_d}{\tau_p}})$$

$$\frac{V_{OH} - V_{OL}}{2} = k V_{in(min)} A_0 (1 - e^{-\frac{t_d}{\tau_p}})$$

$$t_d = 0.693\tau_p$$


$$t_d = \tau_p \ln\left(\frac{2k}{2k - 1}\right)$$

k=ratio between actual and minimum signal


Discriminator propagation delay



 - Propagation delay versus the ratio between the actual and the minimum detectable signal for $\tau_p=100$ ns.



Two stage comp: small signal performance

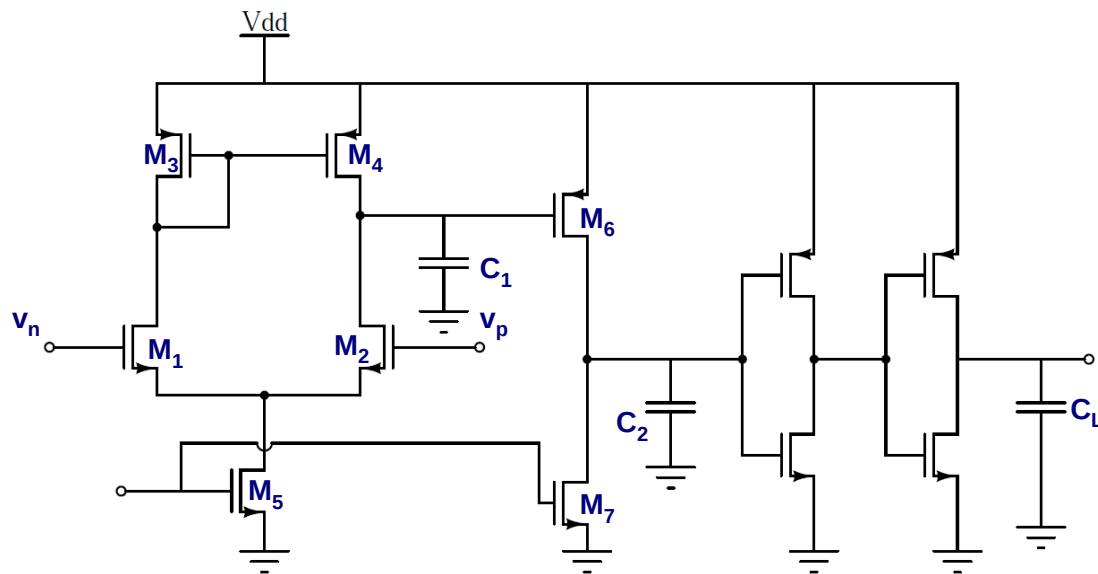

$$\tau_1 = C_1 \frac{1}{g_{ds2} + g_{ds4}}$$


$$\tau_2 = C_2 \frac{1}{g_{ds6} + g_{ds7}}$$

$$A_0 = \left(\frac{g_{m1}}{g_{ds2} + g_{ds4}} \right) \left(\frac{g_{m6}}{g_{ds6} + g_{ds7}} \right)$$

$$A(s) = \frac{A_0}{(1 + s\tau_1)(1 + s\tau_2)}$$

$$v_{out}(t) = A_0 V_{in} \left(1 - \frac{\tau_1 e^{-\frac{t}{\tau_1}}}{\tau_1 - \tau_2} + \frac{\tau_2 e^{-\frac{t}{\tau_2}}}{\tau_1 - \tau_2} \right)$$

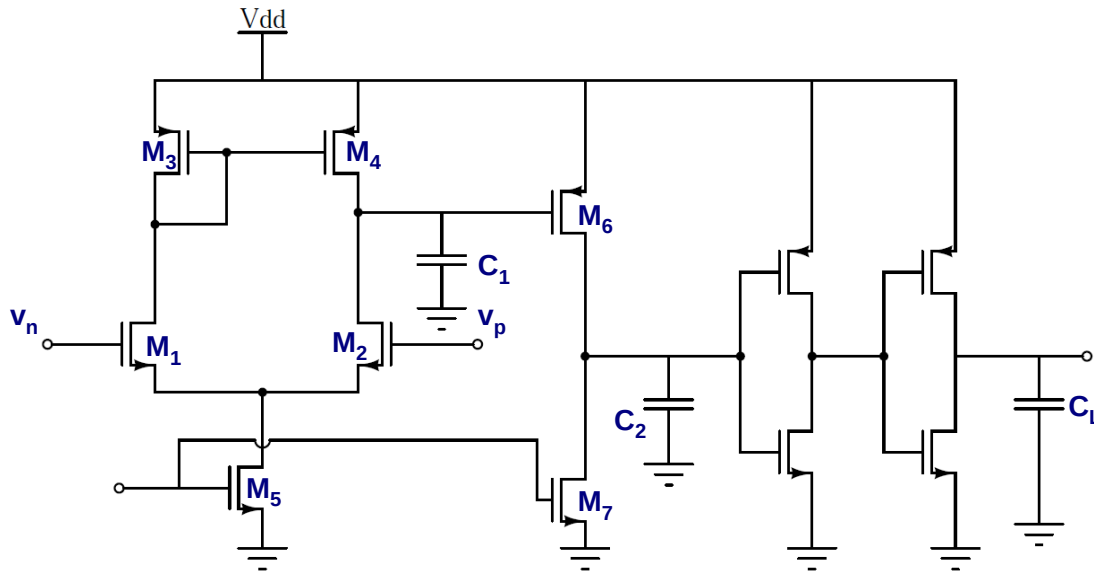Two stage comparator: slew rate limitation




$$SR^+ = \frac{I_6 - I_7}{C_2}$$

$$SR^- = \frac{I_7}{C_2}$$

$$v_{out}(t) = A_0 V_{in} \left(1 - \frac{\tau_1 e^{-\frac{t}{\tau_1}}}{\tau_1 - \tau_2} + \frac{\tau_2 e^{-\frac{t}{\tau_2}}}{\tau_1 - \tau_2} \right)$$

- If the **slope** of the small signal step response **exceeds the SR+ or SR-**, the circuit becomes **slew rate limited** and the output is a ramp with the slope defined by SR⁺ and SR⁻

Comparator with hysteresis

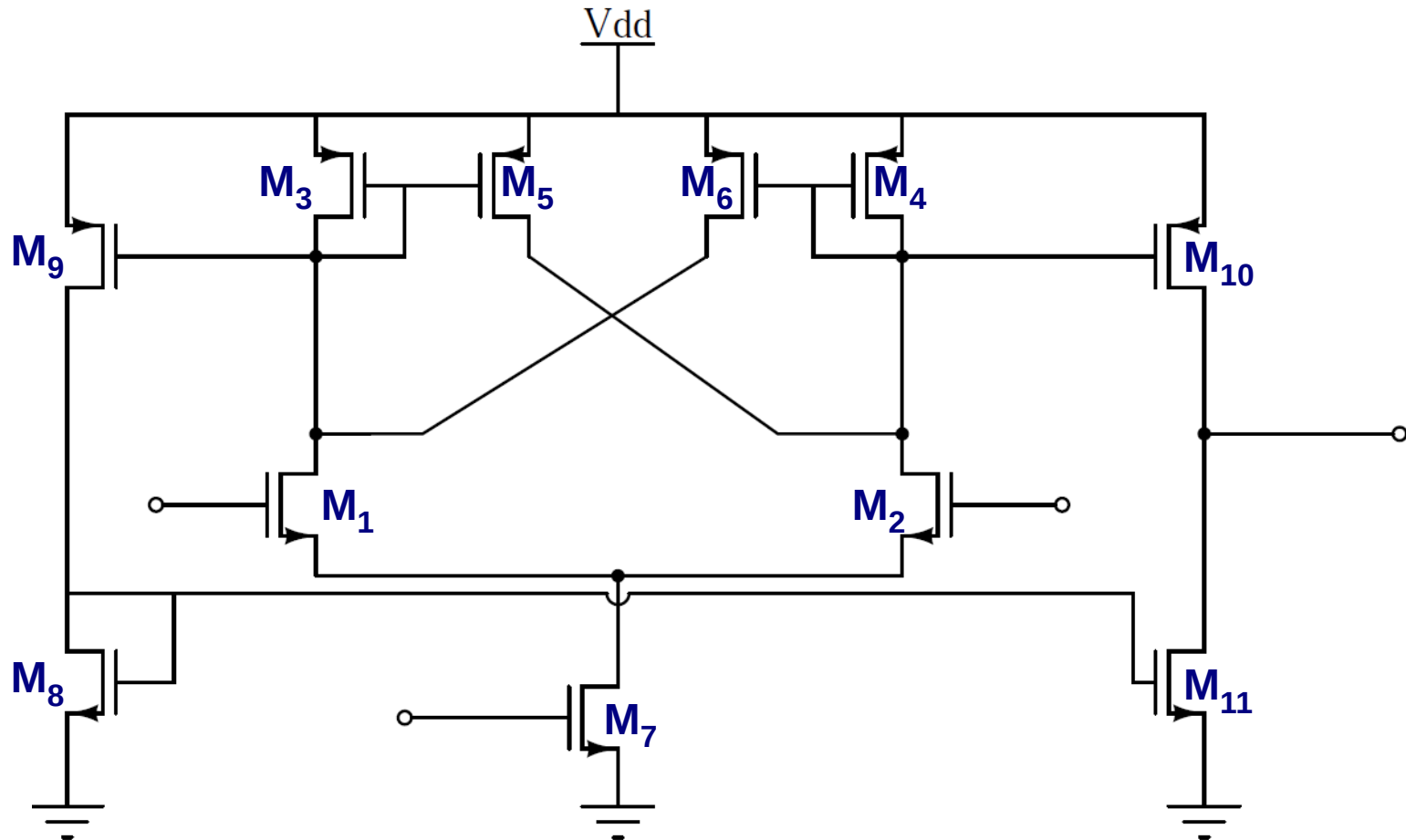


- Hysteresis implies a **positive feed-back** into the circuit.
- M5 and M6 provides the positive feed-back which is **regulated by sizing** M5 and M6 w.r.t M3 M4
- Hysteresis avoids **multiple bouncing** near the threshold point.



Multistage comparators

Jan Kaplon and Matt Noy (CERN) : “Front end electronics for silicon strip detectors in 90 nm CMOS technologies: advantages and challenges”, TWEPP 2010,
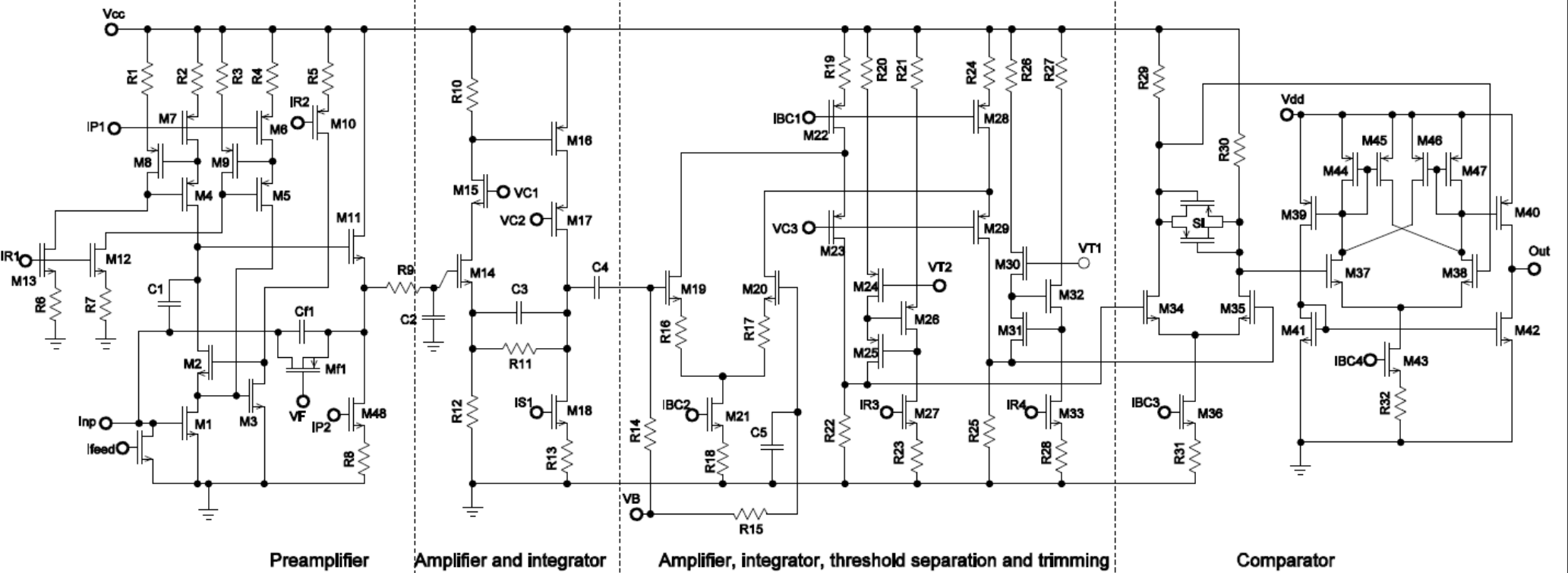
<http://indico.cern.ch/materialDisplay.py?contribId=117&sessionId=15&materialId=slides&confId=83060>




Pre-amplifier

Amp&integrator

Amp, integrator,
threshold, trimming


Comparators

Fast multistage comparators

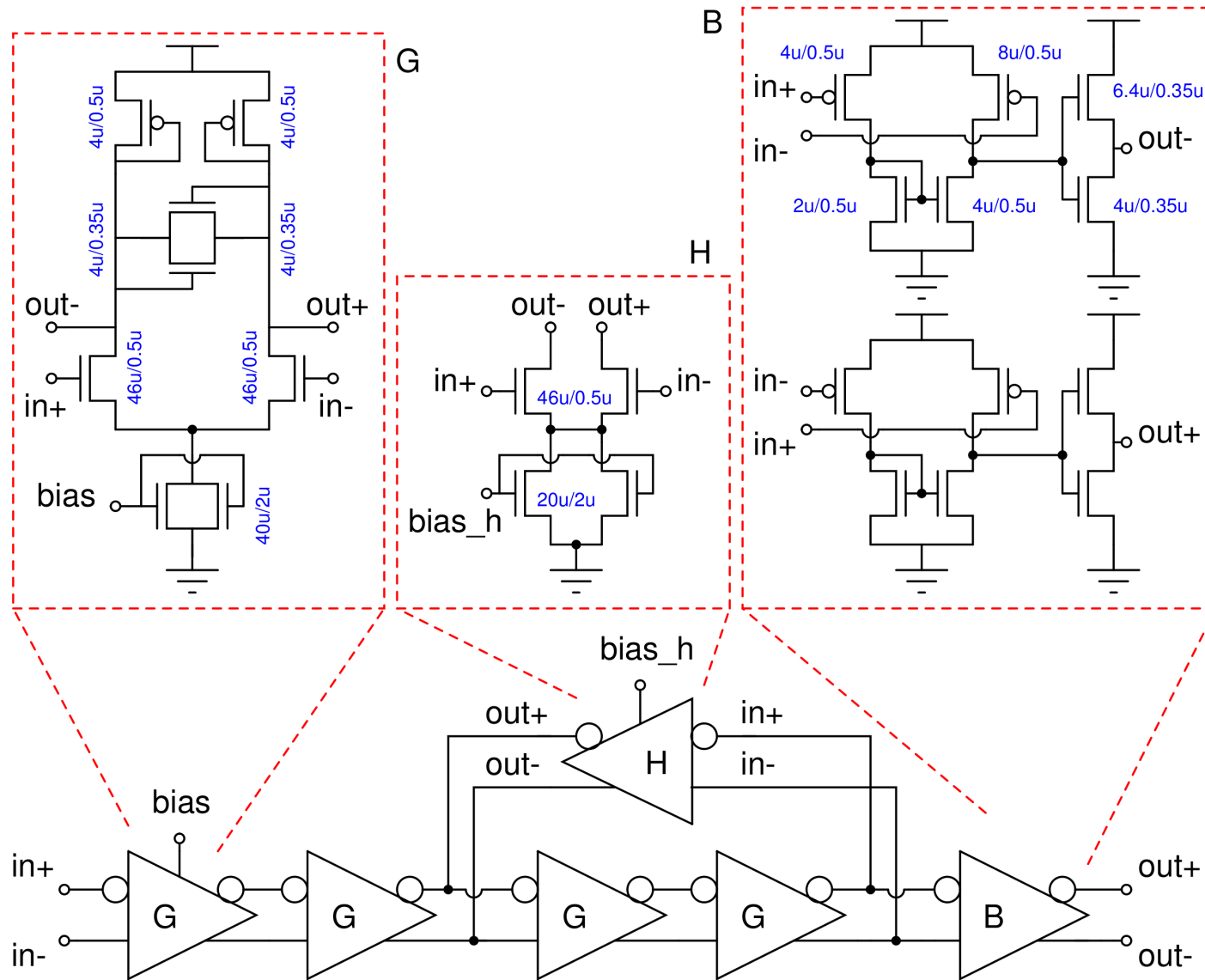

■ **Very fast comparators are obtained by cascading low-gain cells. Full CMOS levels generated only in the last stage.**



Gain cells in multi-stage comparators

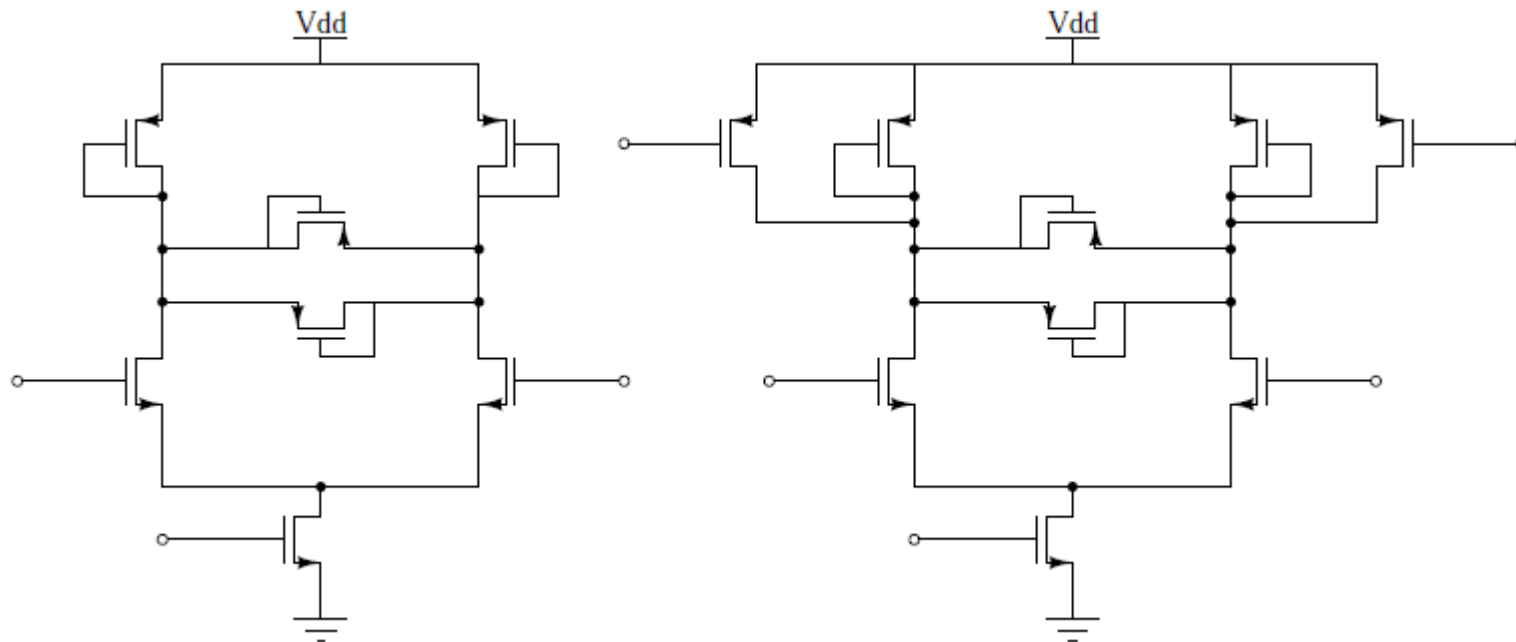

- Differential cells with **diode connected** transistors as load.
- An extra **current source** can be added to **decouple** the equivalent impedance of the **load** from the **gm** of the differential input pair.
- **Diode connected** transistors among the **arms** of the diff pairs avoid **excessive swing** under **overdrive** condition that would slow the **recovery** of the circuit
- **PMOS** transistors could be used also in **triode** region.



Gain cell with resistive loads

 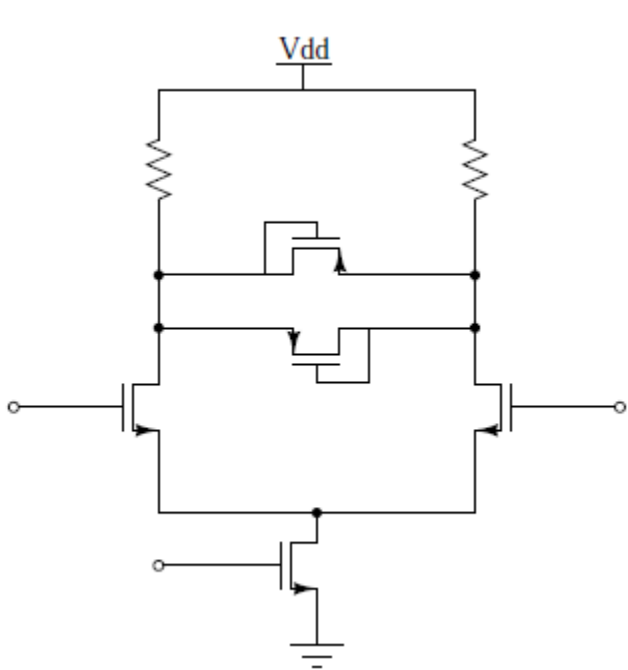

- The **load** can be implemented also with **passive resistors**.
- In deep submicron technologies, these may offer **less parasitic capacitance** and give better speed.
- At low supply voltage (typical of modern CMOS technologies) look carefully at the **variation of bias points** with resistor change due to **process variations**.
- Cascoding can be applied to any of the cells.

How many stages?



$$A_0 = G^{1/n}$$

$$GBW = \frac{A_0}{\tau}$$

$$t = n\tau = \frac{nG^{1/n}}{GBW} \quad \frac{dt}{dn} = 0 = \frac{G^{1/n}(n - \ln(G))}{nGBW} = 0$$

$$n = \ln G \quad A = e$$

- **A_0 and GBW** are the **gain** and **gain-bandwidth** product of the **individual** cell. **G** is the total **gain** of the **full chain** and **n** the **number of stages**.
- Example: gain of **2500** (necessary to resolve 0.5 mV to 1.2 V) number of stages=8
- **High speed** lead quickly to **high power**.
- Usually a compromise needs to be found.



IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 24, NO. 2, APRIL 1989

Design example of multi-stage comparator



F. Anghinolfi et al. "NINO, an Ultrafast Low-Power Front-End Amplifier Discriminator for the Time-of-Flight Detector in the ALICE Experiment", IEEE Trans. Nucl. Sci., vol. 51, n. 5 October 2004, pp. 1974-1978

Parameter	Value
Peaking time	1ns
Signal range	100fC-2pC
Noise (with detector)	< 5000 e- rms
Front edge time jitter	< 25ps rms
Power consumption	30 mW/ch
Discriminator threshold	10fC to 100fC
Differential Input impedance	$40\Omega < Z_{in} < 75\Omega$
Output interface	LVDS

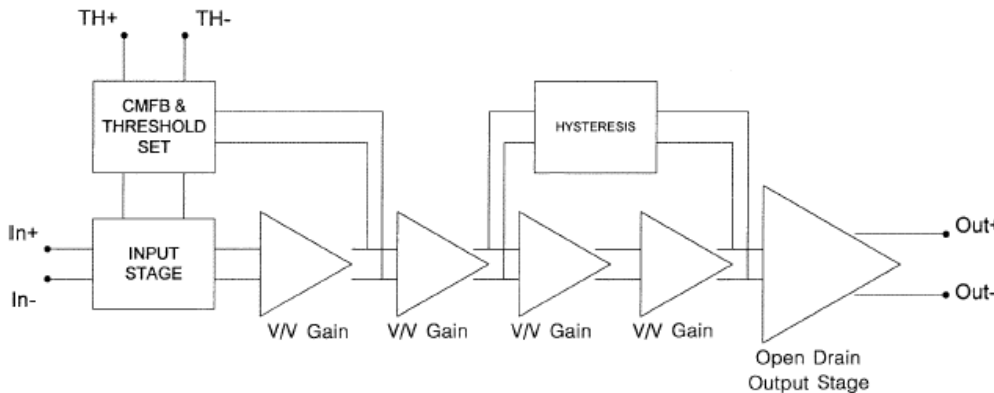
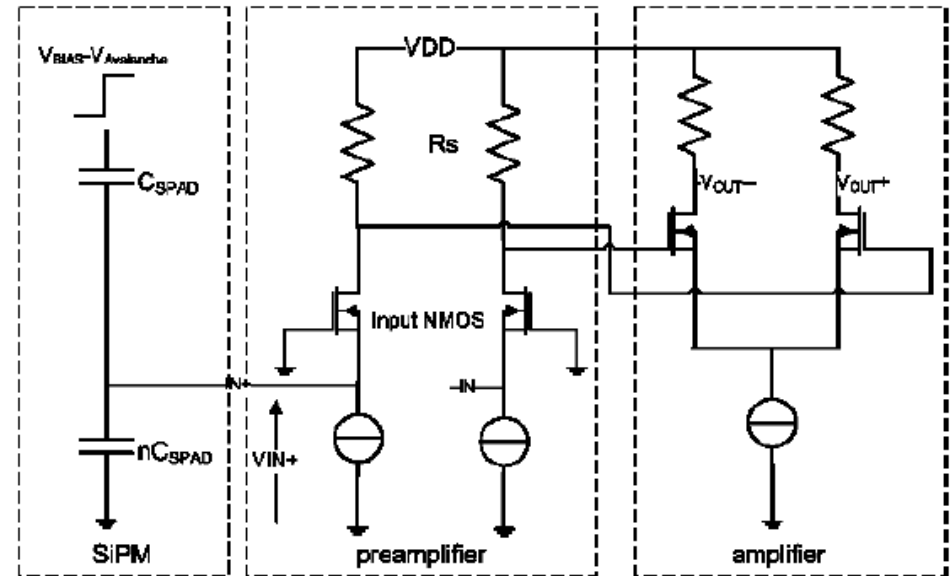


Technology: 0.25 μ m CMOS

Current mode front-end and comparator



 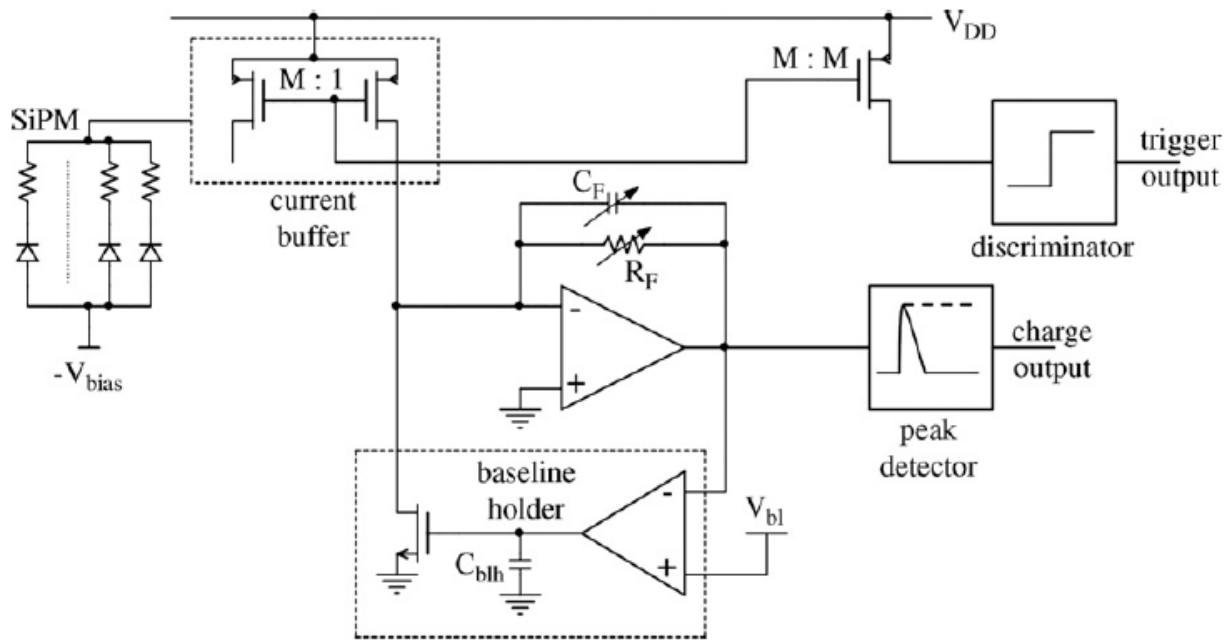A. Argentieri, et al., Nucl. Instr. and Meth. A (2010), doi:10.1016/j.nima.2010.08.067



Current comparators:


E. Traff, “**Novel Approach to High Speed CMOS Current Comparators**”

Electronics Letters, 30th January 1992, vol. 28, n.3

A.T.K. Tang and C. Toumazou, “**High Performance CMOS Current Comparator**”

Electronics Letters, 6th January 1994, vol. 30, n.1

Discrete-time (latched) comparator

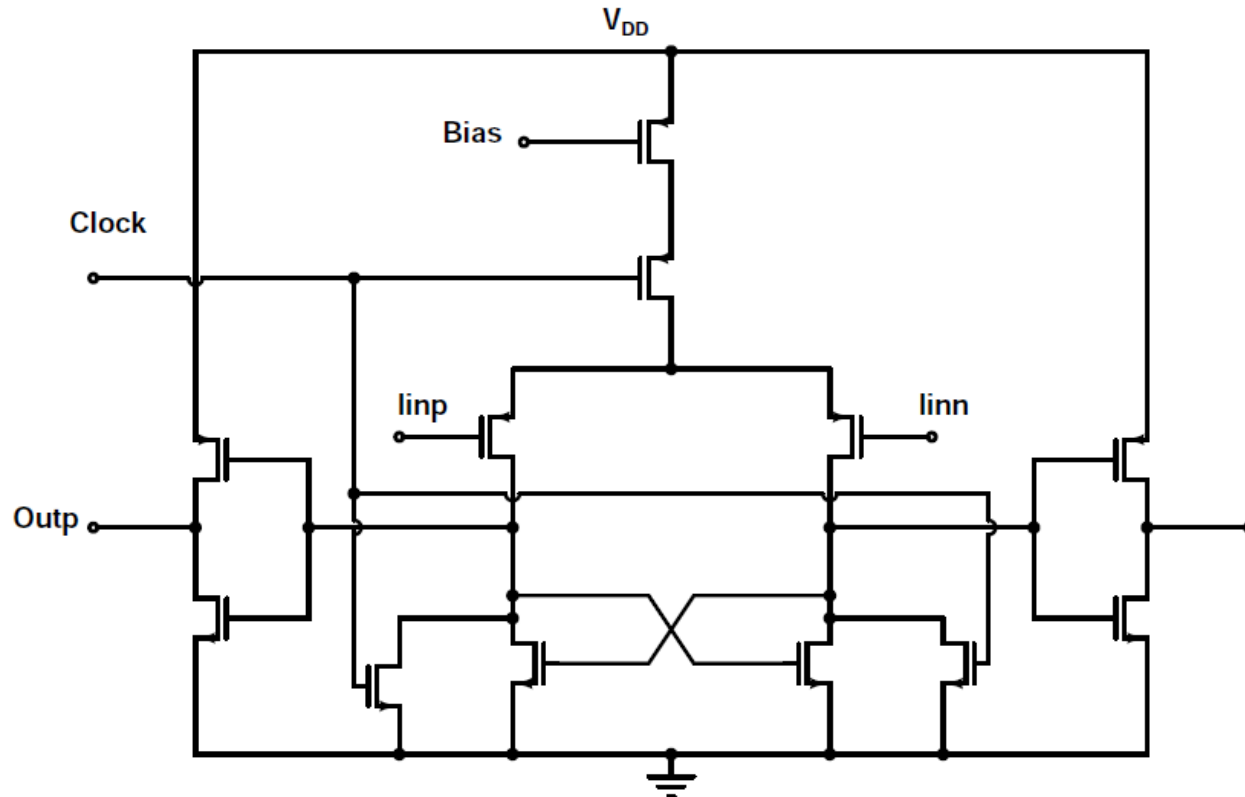

- Exploit positive feed-back to make a very fast decision.
- Very good sensitivity.
- The standard in ADC design
- Not often used in front-end as the time of arrival is not known and the switching noise can couple to the preamp.


- Mismatch between transistors in a differential pair originate offset: the effective threshold is different from the imposed one.
- Offset is random.
- Front-end ASIC are multi-channel systems: effective threshold will change from channel to channel
- If a single threshold value is used for all the threshold must be set so that the channel with the lowest threshold does not fire on noise.
- Channels with higher effective threshold will suffer inefficiency.
- The threshold can be tuned on a channel by channel basis, introducing a digital to analog converter in every channel



Example of threshold tuning




473 electrons rms

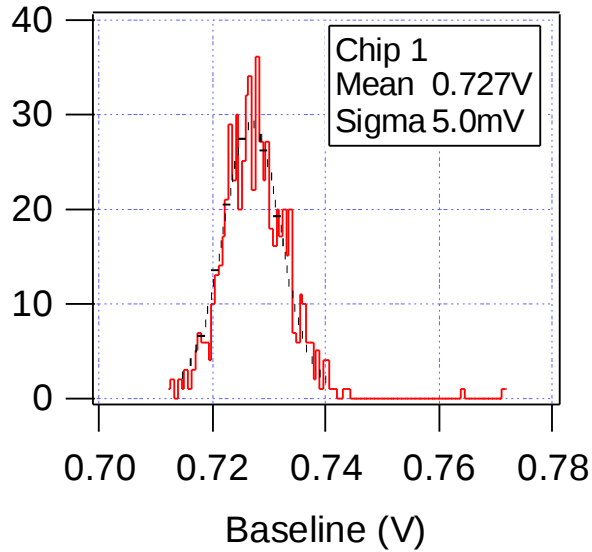


→ **DAC correction** →

62 electrons rms

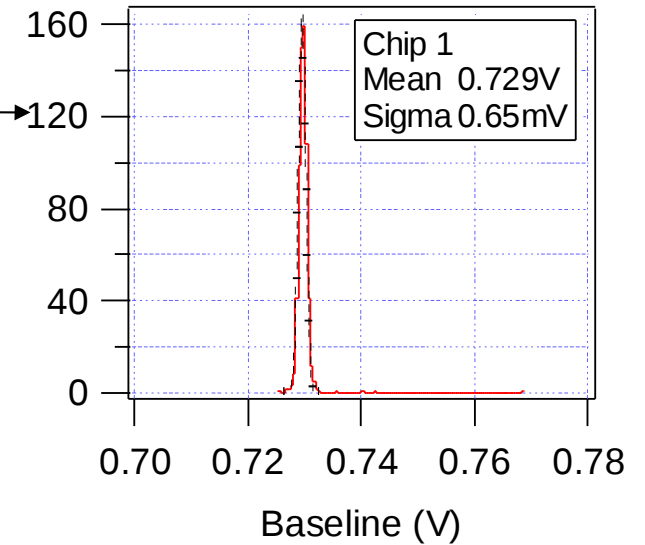


ENC=110 electrons rms

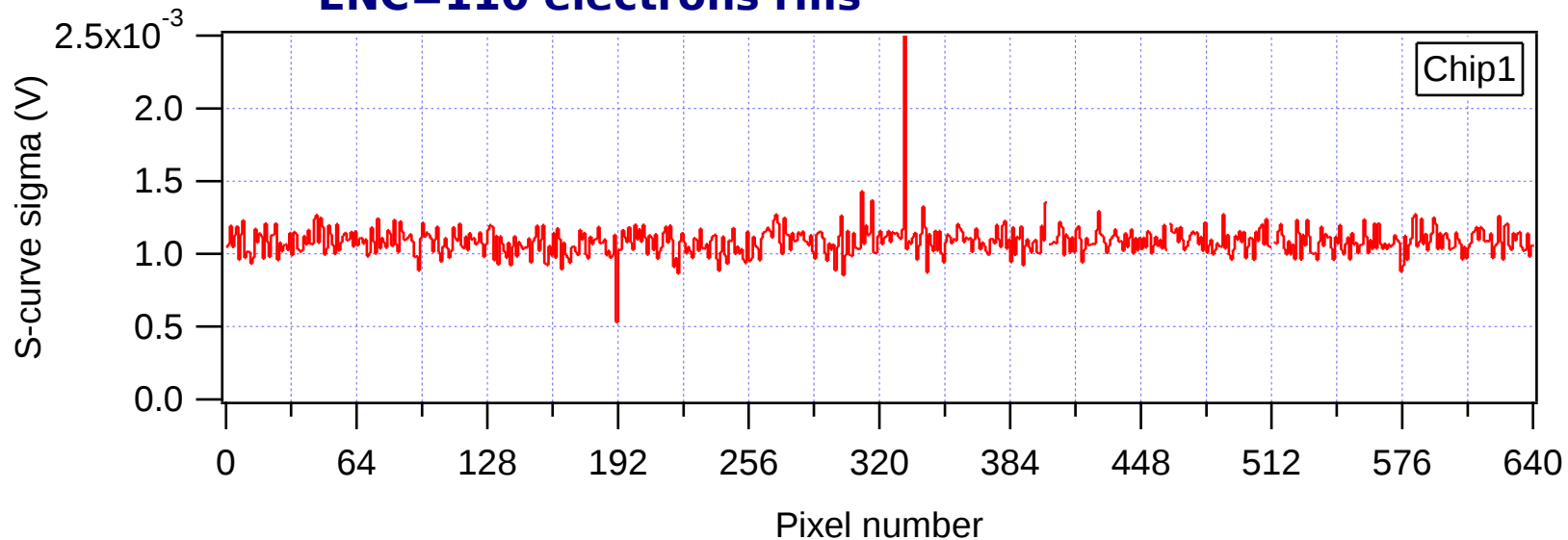



Autozeroing

 

$$V_{OSR} = \frac{\Delta Q}{A_{01}C} + \frac{V_{OSL}}{A_{01}A_{02}} + \frac{V_{OSA2}}{A_{01}(1 + A_{02})}$$



- Offset can be suitably stored on capacitors and subtracted.
- Due to the leakage of the switches, the procedure must be repeated from time to time
- Very small residual offset can be achieved.

- Offset need to be studied with statistical simulations (Monte Carlo)

Error in timing measurement: jitter



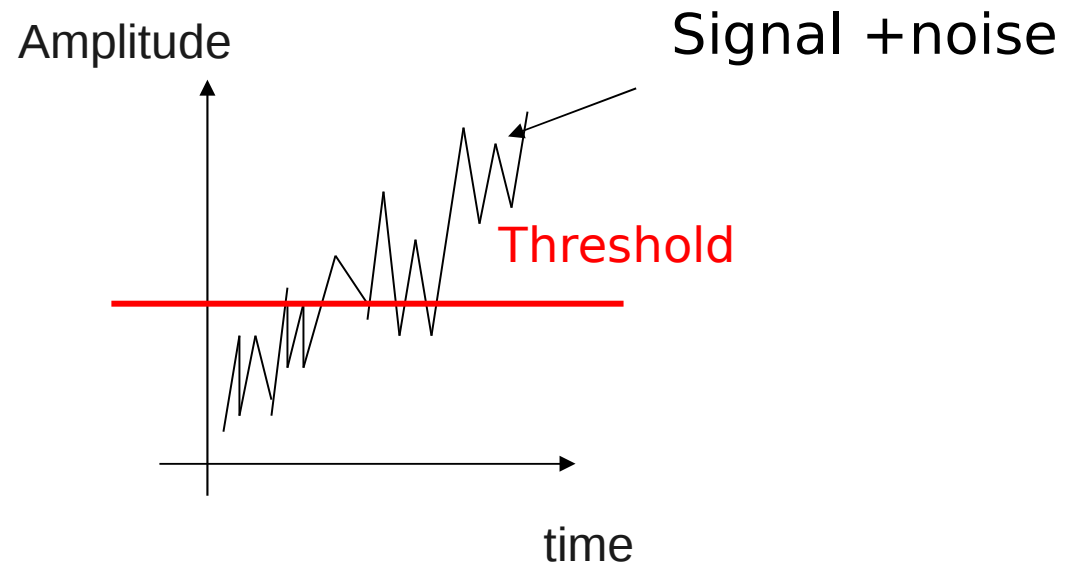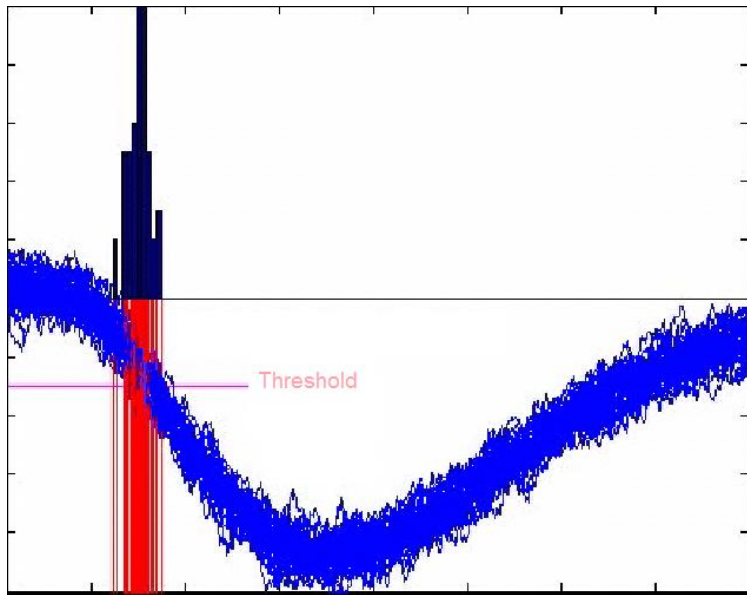- Jitter is how noise before the discriminator appears in the time domain



JFG pictures...

$$\sigma_t = \frac{\sigma_n}{\left(\frac{dV}{dt}\right)}$$

Proportional to the sqrt of the bandwidth


Proportional to the bandwidth



Jitter vs signal amplitude



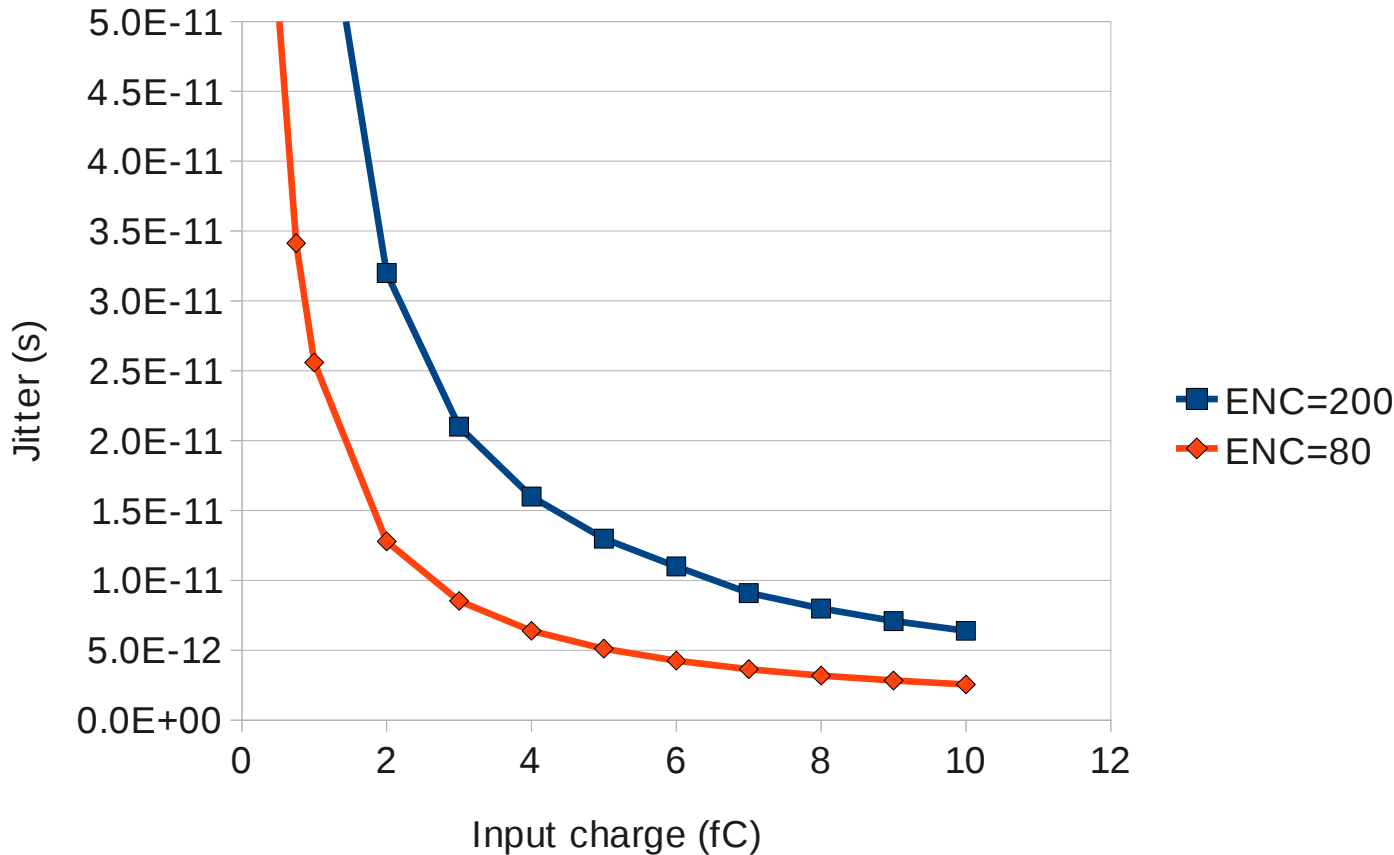- For a total signal rise time of **2 ns**, a **10 ps** resolution can be reached with a noise of **200** electrons and a signal of **6 fC** or a signal of **2.5 fC** and a noise of **80** electrons.



$$\sigma_t = \frac{\sigma_v}{\frac{dV}{dt}}$$



An important point



$$SNR = \frac{\sigma_n}{A_{peak}}$$

$$\sigma_t = \frac{\sigma_n}{\frac{dA}{dt}}$$

$$\sigma_n = \propto \sqrt{BW}$$


$$\frac{dA}{dt} = \propto BW$$

$$\sigma_t = \propto \frac{1}{\sqrt{BW}}$$


Timing system need to be fast!



Dual path system

 


- **Leading edge timing is affected by time-walk**
- **Signal with the same shape and different amplitude cross the threshold at different times.**
- **Time walk is a deterministic effect.**
- **It can be corrected by measuring the delay vs amplitude curve and registering also the signal amplitude.**
- **Time over Threshold is an effective way of registering the amplitude, as it re-uses the same hardware for time measurement (discriminator+TDC, no need for additional ADC).**
- **However calibration of the delay-vs-amplitude curve can be cumbersome.**

 


Leading edge timing

Timing discriminators: zero crossing

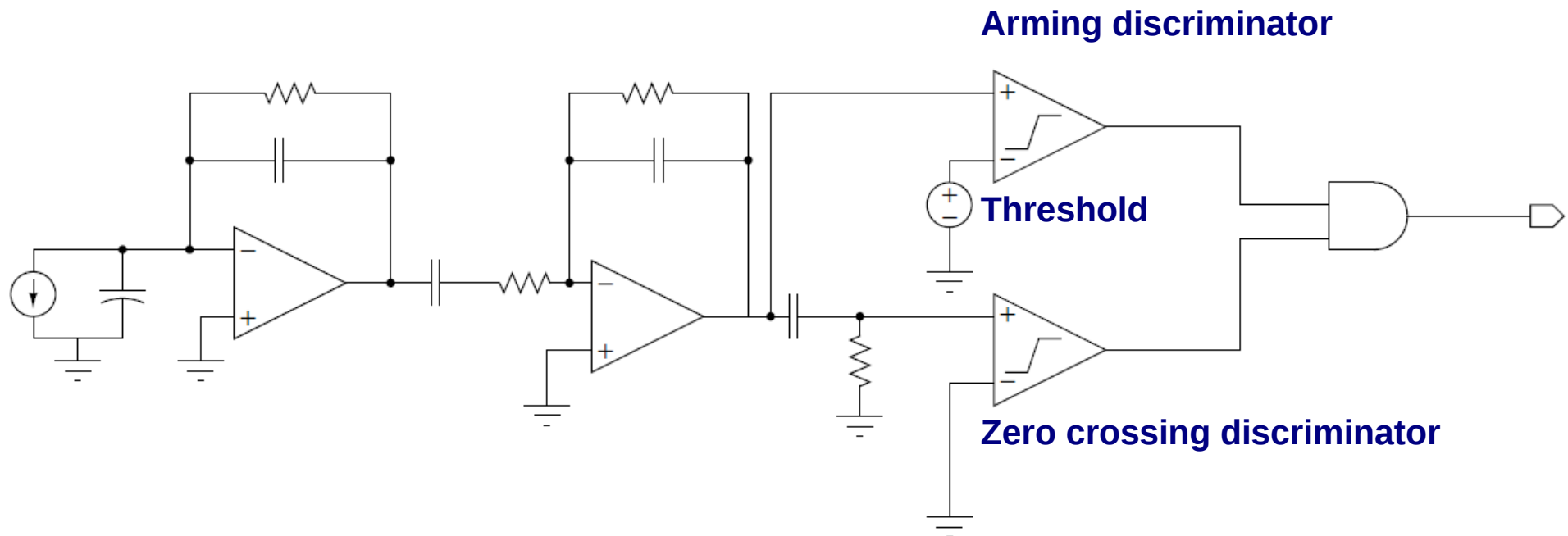

- Operates on a **bipolar** signal.
- The **zero crossing** of the bipolar signal provides the timing.
- Needs to be **gated** to avoid continuous firing on **noise**.
- In IC with a large number of channels **gating** need to be implemented **carefully** (avoid the zcd generates **full swing digital** signals on noise).
- **Insensitive to time-walk**
- **Sensitive to pulse shape variations.**

Timing discriminators: constant fraction

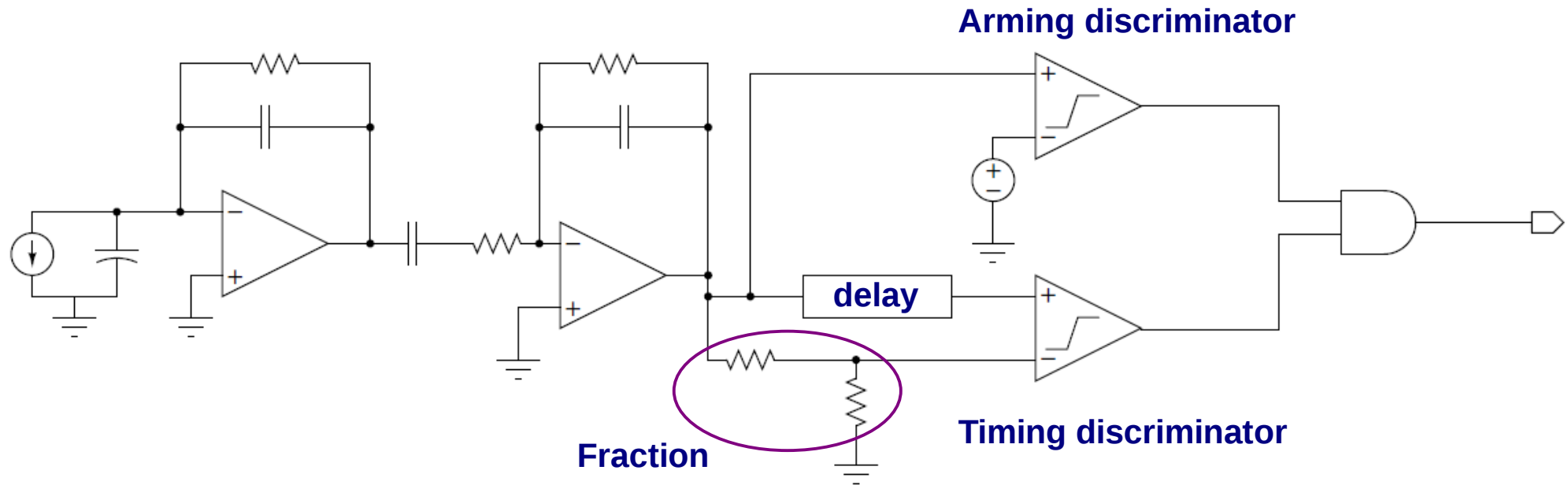


- Comparison between a **delayed copy** of the signal and an **attenuated** one.
- Detection of a **zero crossing** of a **bipolar waveform** (like in zero crossing).
- The key **difference** is how the **bipolar waveform** is **generated**.
- In IC, the **delay line** is often approximated with **RC filters**.
- **Insensitive** to amplitude variations.
- Can **reduce** significantly the sensitivity to **pulse shape variations** if properly optimized.
- **Precise timing** relies on **analog signal processing**. Can give very good performance, but not trivial to implement and a **lot of details** need to be watched out.

Timing discriminators: ideal constant fraction



$$V(t) = \frac{t}{t_r} V_0$$

 

$t_d > t_r$, amplitude compensation only

$$fV_0 = \frac{t - t_d}{t_r} V_0$$

$$t_{zc} = ft_r + t_d$$

$t_d > t_r$, amplitude and rise time compensation

$$f \frac{t}{t_r} V_0 = \frac{t - t_d}{t_r} V_0$$

$$t_{zc} = \frac{t_d}{1 - f}$$




CFD timing with more realistic signal



$$\frac{t - t_d}{\tau} e^{-\frac{t-t_d}{\tau}} - f \frac{t}{\tau} e^{-\frac{t}{\tau}} \quad t_{z_c} = \frac{t_d e^{t_d/\tau}}{e^{t_d/\tau} - f}$$

 
Waveform obtained from a CR-RC with 5 ns peaking time and a delay of 2ns.



Effect of delay and fraction




Amplitude

 

Obtained from **CR-RC** with **5 ns** peaking time and a delay of **4ns**, fraction = **0.5**

Amplitude

 


Obtained from **CR-RC** with **5 ns** peaking time and a delay of **4ns**, fraction = **0.2**

CFD with integrated delay line



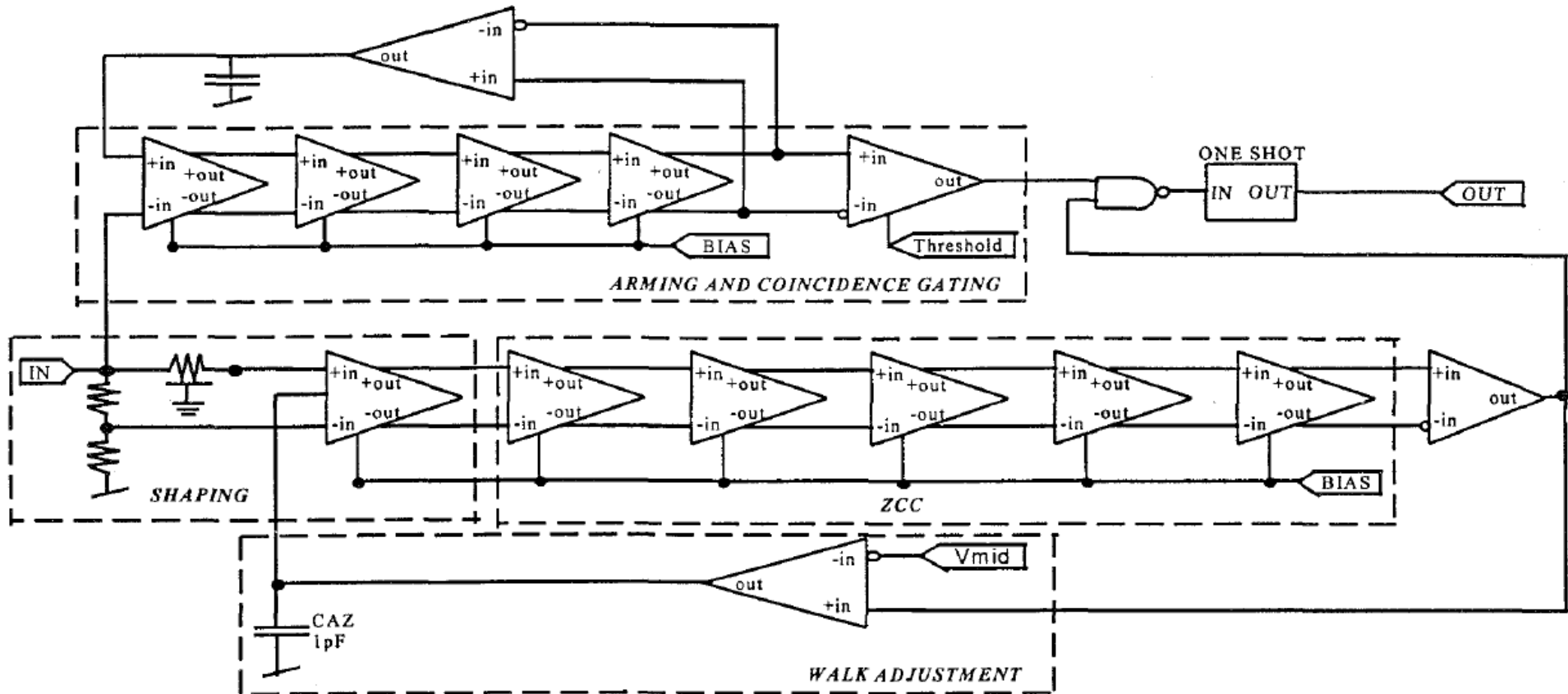M. L. Simpson, G. R. Young, R.G. Jackson and M. Xu, "A Monolithic, Constant Fraction Discriminator Using Distributed R-C Delay Line Shaping", *IEEE Trans. Nucl. Sci.*, vol. 43, no. 3, June 1996, pp. 1695-1699.



- Comparators based on chain of **large bandwidth, low gain** cells.
- Automatic **offset compensation** with servo-loop.
- Fraction: resistive voltage divider
- Delay line: on silicon **integrated delay line**.




Integrated delay line implementation



M. L. Simpson, G. R. Young, R.G. Jackson and M. Xu, "A Monolithic, Constant Fraction Discriminator Using Distributed R-C Delay Line Shaping", *IEEE Trans. Nucl. Sci.*, vol. 43, no. 3, June 1996, pp. 1695-1699.

 Delay line area:
 $90\ \mu\text{m} \times 69.6\ \mu\text{m}$




- Delay line implemented as **poly serpentine** over a poly **backplane**.
- Today IC process may offer **delay lines** as a **library component** (so well **modeled**)
- Implementation of **longer delay** require considerable **space** (O(1 mm)) for 4 ns delay.
- More common **alternative**: replace the delay line with a **multi-pole RC** filter.

Lumped filters: single pole high-pass

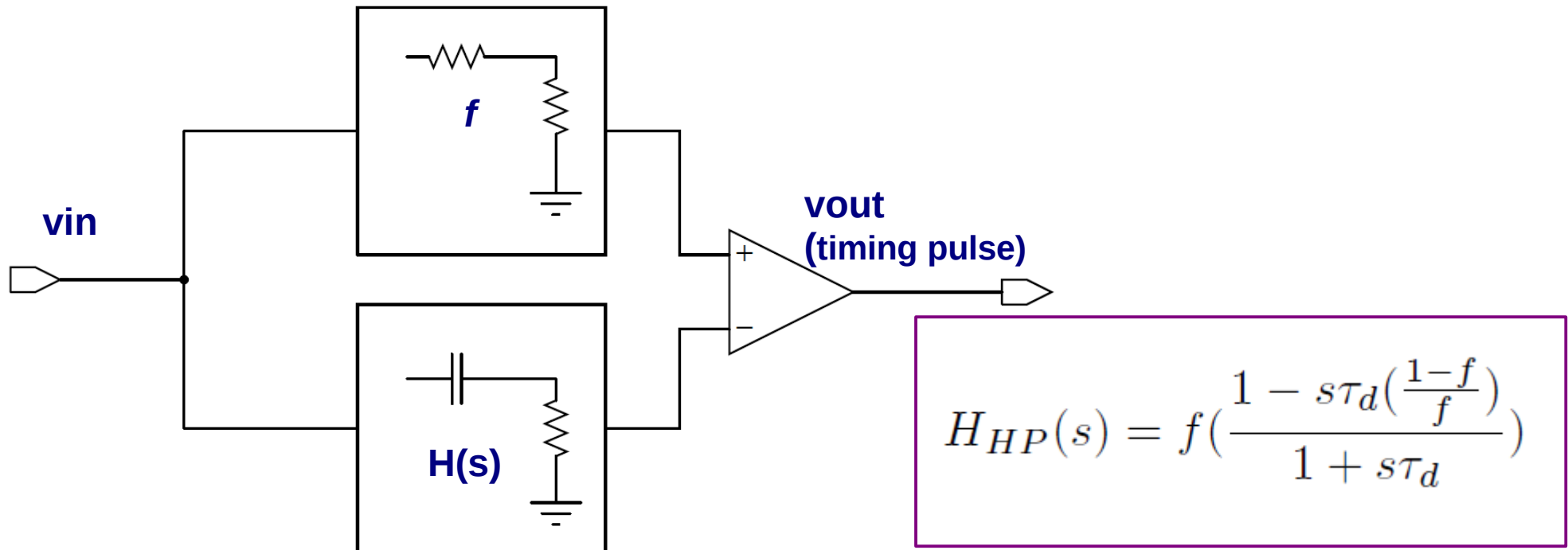C. H. Nowlin, "Low-noise lumped element timing filters with rise-time invariant cross-over time", Rev. Sci. Instr. 63 (4), April 1992, pp. 2322-2326.

David M. Binkley, "Performance of Non-Delay-Line Constant Fraction Discriminator Timing Circuit", *IEEE Trans. Nucl. Sci.*, vol. 41, no. 4, August 1994, pp. 1169-1175.




- The **zero** in the transfer function is necessary to provide the **bipolar** signal for timing.
- The discriminator provides **amplitude compensation** of **time walk**.
- Zero crossing is **independent** from input **rise time** only for inputs with **linear rising edge** and constant slope

Lumped filters: single pole low-pass



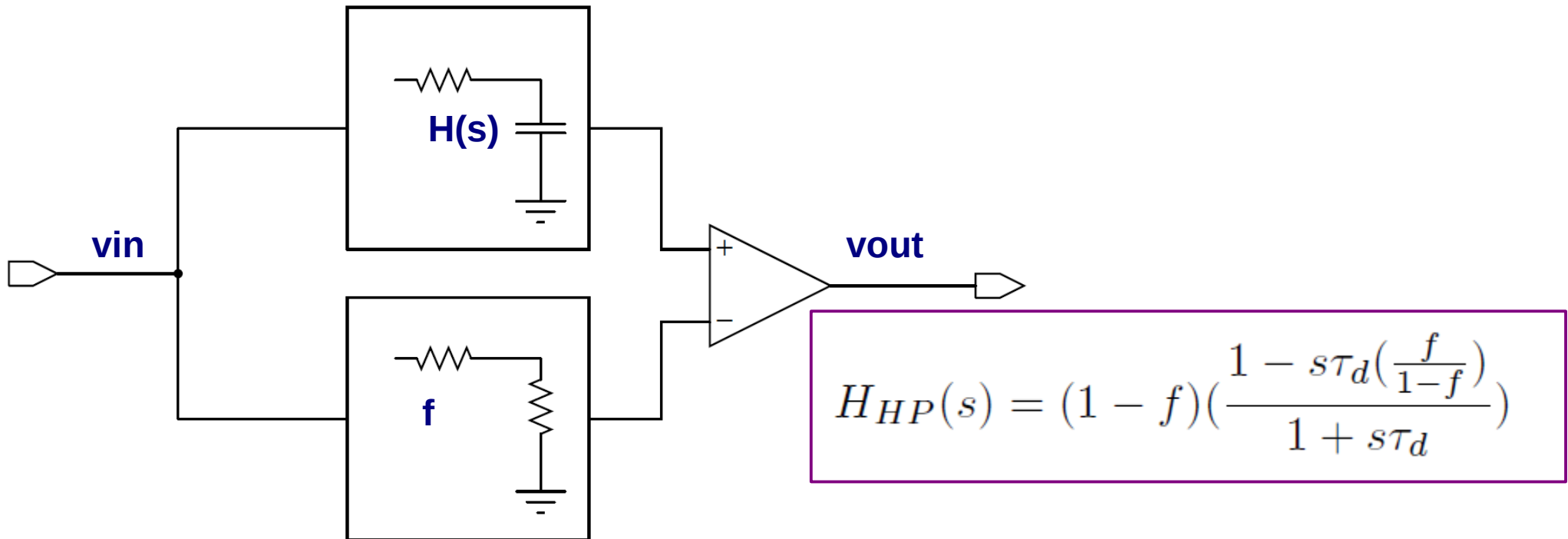David M. Binkley, "Performance of Non-Delay-Line Constant Fraction Discriminator Timing Circuit", *IEEE Trans. Nucl. Sci.*, vol. 41, no. 4, August 1994, pp. 1169-1175.



- The **zero** in the transfer function is also provided even a **low pass filter** is used for the delay.
- The discriminator provides **amplitude compensation** of **time walk**.
- Zero crossing is **independent** from input **rise time** only for inputs with **linear rising edge** and constant slope
- The transfer function is identical to the one of the previous circuit if $f=0.5$. Otherwise it can be made identical by changing f in $1-f$.

Lumped filters: higher order low pass filters



David M. Binkley, "Performance of Non-Delay-Line Constant Fraction Discriminator Timing Circuit", *IEEE Trans. Nucl. Sci.*, vol. 41, no. 4, August 1994, pp. 1169-1175.

Circuit Configuration		Normalized Circuit Performance					
Topology	Delay (tau ea.)	Fraction	Under-drive	Over-drive	Zero-Cross Slope	Output Noise	Timing Jitter
	$\frac{t_d}{t_{in}}$	(f)	$\frac{V_{und}}{V_{inpk}}$	$\frac{V_{ovr}}{V_{inpk}}$	$\frac{K_{zero}}{K_{inpk}}$	$\frac{\sigma_{vcf}}{\sigma_{vin}}$	$\frac{\sigma_{icf}}{\sigma_{tin}}$
Delay Line	1.805	0.2	-0.167	0.8	0.8	0.987	1.234
Gaussian, 1-pole	1.770	0.5	-0.157	0.5	0.176	0.500	2.861
Gaussian, 2-pole	0.749	0.5	-0.201	0.5	0.245	0.611	2.492
Gaussian, 3-pole	0.477	0.5	-0.225	0.5	0.287	0.666	2.316
Gaussian, 4-pole	0.351	0.5	-0.242	0.5	0.318	0.701	2.204

Input signal is 1-pole lowpass-filtered step input with time-constant t_{in} .
Zero-crossing time (t_{cf}) is at $2t_{in}$.


Circuit Configuration		Normalized Circuit Performance					
Topology	Delay (tau ea.)	Fraction	Under-drive	Over-drive	Zero-Cross Slope	Output Noise	Timing Jitter
	$\frac{t_d}{t_{in}}$	(f)	$\frac{V_{und}}{V_{inpk}}$	$\frac{V_{ovr}}{V_{inpk}}$	$\frac{K_{zero}}{K_{inpk}}$	$\frac{\sigma_{vcf}}{\sigma_{vin}}$	$\frac{\sigma_{icf}}{\sigma_{tin}}$
Delay Line	1.503	0.2	-0.126	0.8	0.852	0.994	1.109
Gaussian, 1-pole	1.325	0.5	-0.101	0.5	0.332	0.500	1.506
Gaussian, 2-pole	0.563	0.5	-0.131	0.5	0.446	0.600	1.344
Gaussian, 3-pole	0.360	0.5	-0.148	0.5	0.510	0.648	1.271
Gaussian, 4-pole	0.265	0.5	-0.159	0.5	0.551	0.677	1.228

Input signal is 2-pole lowpass-filtered step input with time-constant t_{in} ($t_{in}/\sqrt{2}$ each pole).
Zero-crossing time (t_{cf}) is at $2t_{in}$.

- Lumped filters **slow-down** the signal decreasing its **slope**, leading to an increase in **jitter**.
- **Increasing the order** of the filter improves the **slope** to delay ratio.
- The **jitter** of a non-delay line CFD with a 4th order filter is only **11% above** the one of the CFD with delay line.
- Fraction of 0.5 is optimal from the **jitter** point of view.

ARC timing

 Robert L. Chase "Pulse Timing System for Use with Gamma Rays on Ge(Li) Detectors" The Review of Scientific Instrumentation, vol. 39, no. 9, September 1968.



Linear rising edge, low pass filtered

$$V_{in} = K\tau[(t/\tau) - 1 + e^{-t/\tau}]$$

Timing signal for pulse with constant slope (blue curve)

$t < t_1$

$$V_{bp} = K\tau f \left[\frac{1}{f} \left(\frac{t - \tau_d}{\tau} - 1 + e^{-(t-\tau_d)/\tau} \right) - (t/\tau - 1 + e^{-t/\tau}) \right]$$

Timing signal for pulse with slope change at t_s (red curve)

$$V_{bp} = K\tau f \left[\frac{1}{f} \left(\frac{t - \tau_d}{\tau} - 1 + e^{-(t-\tau_d)/\tau} \right) - (t/\tau - 1 + e^{-t/\tau}) \right] -$$


$$- V_{bp} = \frac{K\tau}{f} \left[f \left(\frac{t - \tau_d}{\tau} - 1 + e^{-(t-\tau_d)/\tau} \right) - (t/\tau - 1 + e^{-t/\tau}) \right]$$



CFD design example (1)




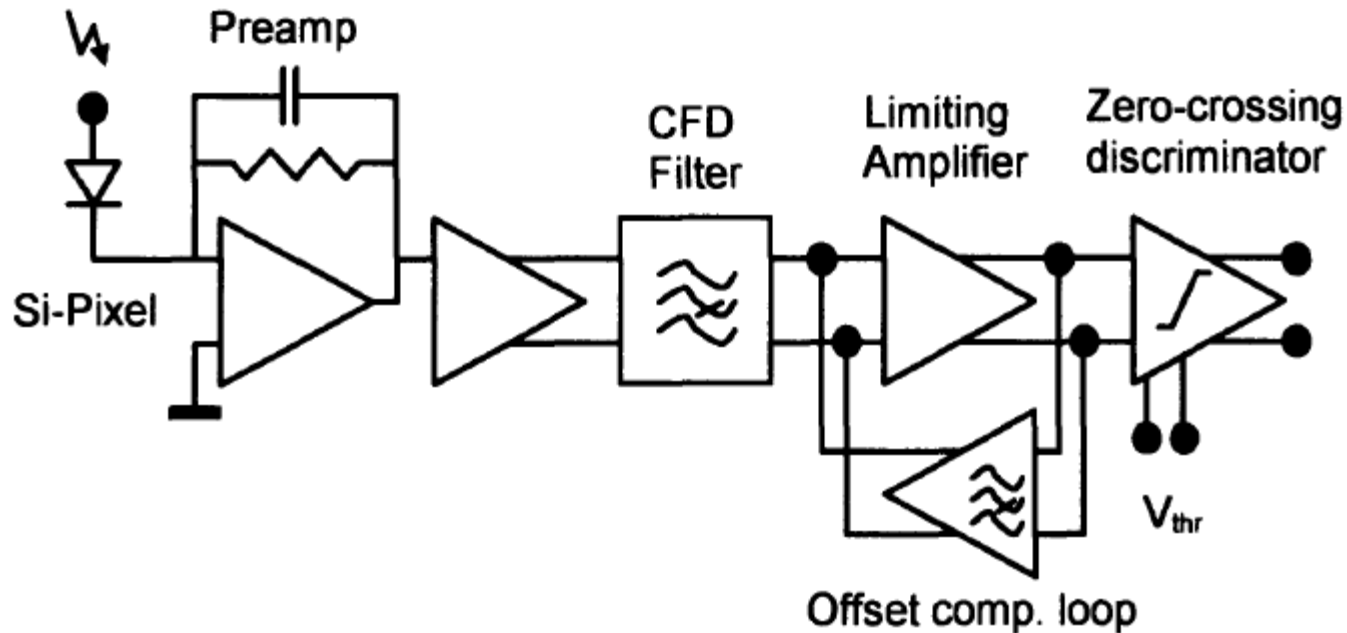S. Martoiu et al, "A Low-Power Front-End Prototype for Silicon Pixel Detectors with 100 ps Time Resolution"
2008 IEEE NSS Conference Record, N44-5



- Technology: **CMOS 0.13 μm , 1.2 V** power supply.
- Dynamic range **10:1**
- Voltage mode operation, **fully differential** topology
- Total area: **280 μm x 80 μm .**

CFD design example (2)

 


- Technology: **CMOS 0.13 μm , 1.2 V** power supply.
- Dynamic range **10:1**
- Voltage mode operation, **fully differential** topology
- Total area: **280 μm x 80 μm .**



CFD design example (3)



 S. Martoiu et al, "A Low-Power Front-End Prototype for Silicon Pixel Detectors with 100 ps Time Resolution"
2008 IEEE NSS Conference Record, N44-5





Discriminator summary



- Leading edge discriminators need correction for time walk.
- They are essentially part of the more complex zero crossing and constant fraction discriminator.
- Constant fraction discriminators with lumped delay lines may offer similar performance with respect with CFD employing true delay lines
- Filter of higher order (4^{th} - 5^{th}) should be used to implement the delay line
- Post amplification after the filter is almost mandatory to properly drive the decision stages.
- Post amplification minimizes the impact of subsequent stages, but does not improve the noise to slope ratio (both signal and noise are amplified).
- CFD are still sensitive to pulse shape variations if the input pulse has not a linear rising edge.
- Minimization of sensitivity to pulse shape variations require several compromise.
- All CFD analysis assume linear circuits...Pulse distortion can significantly compromise timing.
- In order to have good final performance it is mandatory to have a realistic model of the input signal (including its shape and not only amplitude variations) and run very careful simulation with Monte Carlo analysis and process variations...